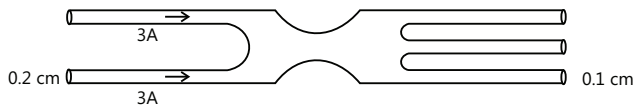


## Solved Examples

### JEE Main/Boards

**Example 1:** 3 A current is flowing through two identical conductors having diameter equal to 0.2 cm. These conductors are then split into three identical conductors each having 0.1 cm diameter (see figure below) Calculate the drift velocities in the thicker and the thinner conductors.



The electron density =  $7 \times 10^{28} \text{ m}^{-3}$ . All the conductors are made of the same material. The electric charge on electron is equal to =  $1.6 \times 10^{-19} \text{ C}$

**Sol:** At the junction the algebraic sum of currents is zero. The drift velocity of charges is the ratio of current density to the charge density.

The current density in the thicker wire

$$= \frac{I}{A} = \frac{3}{\pi r^2} = \frac{3}{\pi(0.1 \times 10^{-2})^2}$$

Current density  $J = nev_d$

$$\therefore V_d = \frac{J}{ne}$$

$$= \frac{3}{\pi(0.1 \times 10^{-2})^2 \times 7 \times 10^{28} \times 1.6 \times 10^{-19}}$$

$$\therefore V_d = 8.5 \times 10^5 \text{ ms}^{-1}$$

6A total current is flowing through the three identical conductors (As per Kirchhoff's First Law).

$\therefore$  The current flowing through each of the wires = 2A

$$\therefore V_d' = \frac{J'}{ne}$$

$$= \frac{2}{\pi \left( \frac{0.1}{2} \times 10^{-2} \right)^2 \times 7 \times 10^{28} \times 1.6 \times 10^{-19}}$$

$$= 2.3 \times 10^{-4} \text{ ms}^{-1}$$

**Example 2:** A potential difference of 200 volt is maintained across a conductor of resistance 100ohm. Calculate the number of electrons flowing through it in one second. Charge on electron,  $e = 1.6 \times 10^{-19} \text{ C}$

**Sol:** Number of electrons flowing per sec, through conductor is the ratio of total charge flowing to the charge of an electron.

Here  $V = 200 \text{ volt}$ ;  $R = 100 \text{ ohm}$ ;

$$e = 1.6 \times 10^{-19} \text{ C}$$

$$\text{Now } I = \frac{V}{R} = \frac{200}{100} = 2 \text{ ampere}$$

Charge flowing in  $t = 1 \text{ sec}$ ,  $q = I t = 2 \times 1 = 2 \text{ C}$

Therefore, number of  $\Omega$  electrons flowing through the conductor flowing in 1 s,

$$n = \frac{q}{e} = \frac{2}{1.6 \times 10^{-19}} = 1.25 \times 10^{19}$$

**Example 3:** A negligibly small current is passed through a wire of length 15 m and uniform cross-section

$$6.0 \times 10^{-7} \text{ m}^2 \quad \rho = \frac{5 \times 6 \times 10^{-7}}{15} = 2 \times 10^{-7} \Omega \text{ m}$$

and its resistance is measured to be  $R = \rho \frac{L}{A}$ .

What is the resistivity of the material at the temperature of the experiment?

**Sol:** The resistance of the conductor is calculated as

$$R = \frac{\rho L}{A}$$

Using  $R = \rho \frac{L}{a}$ , we get  $\rho = \frac{R \times a}{L}$ .


$$\text{i.e. } \rho = \frac{5 \times 6 \times 10^{-7}}{15} = 2 \times 10^{-7} \Omega \text{ m}$$

**Example 4:** Determine the current drawn from 12V supply with internal resistance  $0.5 \Omega$  by the infinite network shown in figure. Each resistance has  $1 \Omega$  resistance.

**Sol:** The equivalent resistance of the circuit is deduced by reducing it to simple network. Using Ohm's law we

get the current through network.

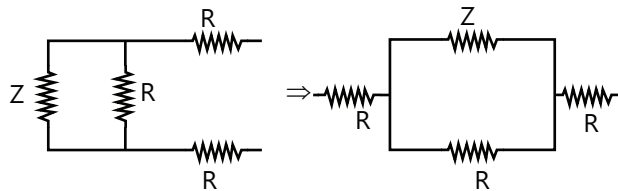Let the total resistance of the circuit be  $Z$  and a set of three resistor of



value  $R$  each be connected to it as shown in the figure, adding of these resistors will not change the value of  $Z$  because the network is infinite then

$$Z = R + \frac{ZR}{Z+R} + R = 2R + \frac{ZR}{Z+R}$$

Or  $Z = 2 + \frac{Z}{1+Z}$  i.e.  $Z^2 - 2Z - 2 = 0$

or  $Z = 1 \pm \sqrt{3}$  or  $Z = 1 + \sqrt{3} = 2.73\Omega$

(value of  $Z$  cannot be negative).

Current drawn,  $I = \frac{E}{Z+r} = \frac{12}{2.73} = 3.71A$

**Example 5:** A wire carries a current of 1.2 A, when a potential difference of 1.8 V is applied across it. What is its conductance? If the wire is of length 3 m and area of cross-section  $5.4 \times 10^{-6} \text{ m}^2$ , calculate its conductivity.

**Sol:** Resistivity is reciprocal of conductivity.

Here  $V = 1.8V$   $I = 1.2 \text{ A}$ ;

$l = 3 \text{ m}$  and  $A = 5.4 \times 10^{-6} \text{ m}^2$  The resistance of wire.

$$R = \frac{V}{I} = \frac{1.8}{1.2} = 1.5\Omega$$

Therefore conductance of wire.

$$G = \frac{1}{R} = \frac{1}{1.5} = 0.67\Omega^{-1}$$

Now,  $R = \rho \frac{l}{A}$  or  $\rho = \frac{RA}{l}$

Also, conductivity of wire,  $\sigma = \frac{1}{\rho}$


Or  $\sigma = \frac{1}{RA} = \frac{3}{1.5 \times 5.4 \times 10^{-6}} = 3.7 \times 10^5 \Omega^{-1} \text{ m}^{-1}$

**Example 6:** Calculate the current flowing through the resistor  $R_1$  in the given circuit.  $R_1 = 10\Omega$ ,  $R_2 = 20\Omega$  and  $R_3 = 30\Omega$  The potentials of the points 1, 2 and 3 are respectively,  $V_1 = 10v$ . Calculate  $V_2 = 6v$  and  $V_3 = 5v$ . Calculate the potential at the junction.

**Sol:** Use the KVL and KCL at junction to get current followed by application of Ohm's law to get value of resistance.

O the junction point in the above circuit (see figure). The potential at point 1, 2 and 3 is higher than the potential existing at points 2 and 3. Hence, the direction of the current is from point 1to O, from O to 2 and from O to point 3. The figure indicates the electric current and their direction.

$$Z = 2 + \frac{Z}{1+Z}$$

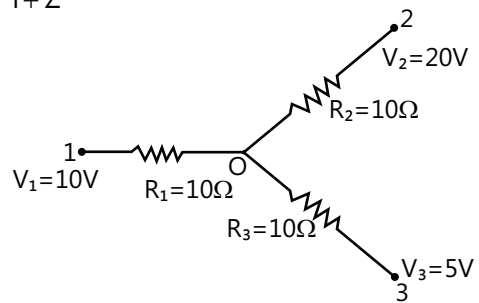


Now for the 1O2 path, we have,

$$V_1 - IR_1 - I_2R_2 = V_2$$

$$\therefore 10 - 10I - 20I_2 = 6$$

$$\therefore 10I - 20I_2 = 4$$

....(i)

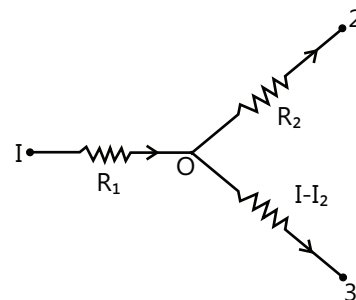

For the 1O3 path, we have

$$10I + 30(I - I_2) = 5$$

$$\therefore 40I - 30I_2 = 5$$

....(ii)

Solving equation (i) and (ii), and we have

$$I = 0.2 \text{ A}$$

Let  $V_0$  be the potential at point O, then

$$10 - V_0 = IR_1$$


$$\therefore 10 - V_0 = 2$$

$$\therefore V_0 = 8V$$

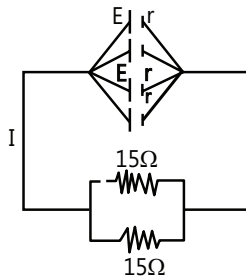**Example 7:** Four identical cells, each of emf 2V, are joined in parallel providing supply of current to external circuit consisting of two  $15\ \Omega$  resistors joined in parallel. The terminal voltage of the cells as read by an ideal voltmeter is 1.6 V. Calculate the internal resistance of each cell.

**Sol:** For parallel connection of  $n$  identical cells, the net emf is equal to that of one cell and the net internal resistance is the parallel combination of resistances of all the cells  $r_{eq} = \frac{r}{n}$ .

Four cells are connected in parallel to the parallel combination of two  $15\ \Omega$  resistors as shown in figure.



Let  $r$  be internal resistance of each cell and  $I$  be the current  $I$  in the circuit. Since the cells are connected in parallel.

Total e.m.f in the circuit – e.m.f. one cell -2V

Further, total internal resistance of the cells is gives by

$$\frac{1}{r'}r = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \frac{1}{r} = \frac{4}{r^4} \text{ or } r' = r/4$$

Let  $R$  be resistance of the parallel combination of two  $15\ \Omega$  resistors. Then, total external resistance,

$$R = \frac{15 \times 15}{15 + 15} = 7.5\ \Omega$$


Now, internal resistance of the parallel combination of cells is given by

$$r' = \left( \frac{E}{V} - 1 \right) R \text{ or } \frac{r}{4} = \left( \frac{2}{1.6} - 1 \right) \times 7.5 \text{ or } r = 7.5\ \Omega$$

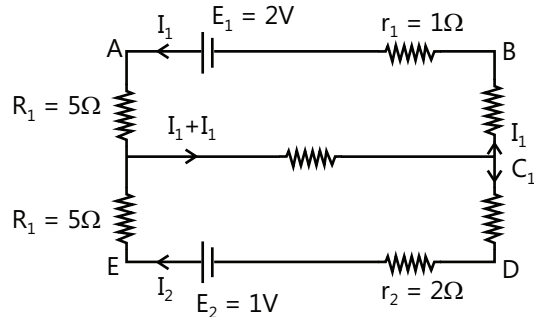**Example 8:** Two cell of e.m.f. 2V and 1 V and of internal resistance  $1\ \Omega$  and  $2\ \Omega$  respectively have their positive terminals connected by a wire of  $10\ \Omega$  resistance and their negative terminals by a wire of  $4\ \Omega$  resistance. Another coil of  $10\ \Omega$  is connected between the middle points of these wires. Find the potential difference across the  $10\ \Omega$  coil.

**Sol:** Use KVL and KCL and solve to get the current through the resistances and total current through the circuit. Use Ohm's law to get the equivalent P.D. across  $R$ .

The positive terminals of the cells  $E_1$  and  $E_2$  are connected to the wire AE of resistance  $10\ \Omega$  and negative terminals to the wire BD of resistance  $4\ \Omega$ . The resistance of  $10\ \Omega$  is connected between the middle points F and C of the wires AE and BD respectively. (See figure)



$$\therefore R_1 = R_2 = \frac{10}{2} = 5\ \Omega; \quad R_3 = R_4 = \frac{4}{2} = 2\ \Omega$$

The distribution of current in various branches is shown in the figure.

In closed part ABCFA of the circuit

$$\begin{aligned} I_1 \times r_1 + I_1 \times R_3 + (I_1 \times I_2)R + I_1 \times R_3 &= E_a \\ \text{or } I_1 \times 1 + I_1 \times 5 + (I_1 \times I_2) \times 10 + I_1 \times 2 &= 2 \\ \text{or } 9I_1 + 5I_2 &= 1 \end{aligned} \quad \dots(i)$$

In closed part CDRFC of the circuit:

$$\begin{aligned} I_2 \times r_2 + I_2 \times R_2 + (I_1 \times I_2)R + I_2 \times R_4 &= E_2 \\ \text{or } I_2 \times 2 + I_2 \times 5 + (I_1 \times I_2) \times 10 + I_1 \times 2 &= 1 \\ 10I_1 + 9I_2 &= 1 \end{aligned} \quad \dots(ii)$$

$$r' = \left( \frac{E}{V} - 1 \right) R$$

Solving equation (i) and (ii) we have

$$I_1 = \frac{14}{121}\ \text{A} \text{ and } I_2 = \frac{1}{121}\ \text{A}$$


Therefore, current through resistance  $R$ ,

$$I_1 + I_2 = \frac{4}{121} + \left[ -\frac{1}{121} \right] = \frac{13}{121}\ \text{A}$$

Potential difference across the resistance  $R$

$$(I_1 + I_2)R = \frac{13}{121} \times 10 = 1.0744\ \text{V}$$

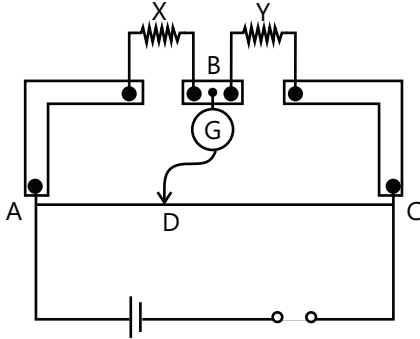**Example 9:** (a) In a meter bridge (See figure), the balance point is found to be at 39.5 cm from the end A, when the resistor Y is of  $12.5\Omega$ . Determine the resistance of X. Why are the connection between resistors in a Wheatstone or Meter Bridge made of thick copper strips?



(b) Determine the balance point of the bridge above if X and Y interchanged.

(c) What happens if the galvanometer and cell are interchanged at the balance point of the bridge?

Would the galvanometer show any current?

**Sol:** For potentiometer circuit,  $E \propto l \Rightarrow R \propto l$ . Thus we take the ratio of resistances.

(a) (i) Using  $X - R \frac{1}{100 - l}$ , we get

$$X = \frac{12.5(39.5)}{(100 - 39.5)} = \frac{12.5(39.5)}{6} = 8.2\Omega$$

(ii) Thick copper strips are used to reduce their resistance because this resistance is not

Accounted for in the calculations.

(b) Interchanging R and X we get

$$R = X \frac{1}{100 - l} \quad \text{i.e. } 100R - Rl = Xl$$

$$\text{i.e. } I = \frac{R100}{R + X} \quad \text{i.e. } I = \frac{12.5 \times 100}{12.5 + 8.2}$$


(c) In this case also the galvanometer will not show current.

**Example 10:** A network of resistors is connected to a 16 V battery with internal resistance of  $1\Omega$ , as shown in figure.

(a) Compute the equivalent resistance of the network.

(b) Obtain the current each resistor.

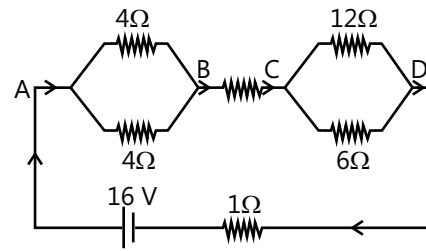(c) Obtain the voltage drops  $V_{AB}$ ,  $V_{BC}$ ,  $V_{CD}$



**Sol:** Compute  $R_{\text{equ}}$  first than compute the current through network. Then use Ohm's law to get P.D. across each arm.

(a) The network is a simple series and parallel combination of resistors. First the two  $4\Omega$  resistors in parallel are equivalent to a resistor  $= \left[ \frac{4 \times 4}{4 + 4} \right] \Omega = 2\Omega$

In the way, the  $12\Omega$  and  $6\Omega$  resistor in parallel are equivalent to a resistor of  $\left[ \frac{12 \times 6}{12 + 6} \right] \Omega = 4\Omega$ .

The equivalent resistance R of the network is obtained by combining these resistors ( $2\Omega$  and  $4\Omega$ ) with  $1\Omega$  in series, that is,  $R = 2\Omega + 4\Omega + 1\Omega = 7\Omega$ .

(b) The total current I in the circuit is

$$I = \frac{E}{R + r} = \frac{16V}{(7 + 1)\Omega} = 2A$$

Consider the resistors between A and B. If  $I_1$  is the current in one of the  $4\Omega$  resistors and  $I_2$  the current in the other,  $I_1 \times 4 = I_2 \times 4$

That is  $I_1 = I_2$ , which is otherwise obvious from the symmetry of two arms.

$$\text{But } I_1 + I_2 = I = 2A. \quad \text{Thus } I_1 = I_2 = 1A$$

That is current in each  $4\Omega$  resistor 1 A. Current in  $1\Omega$  resistor between Band C would be 2 A.

Now consider the resistance between C and D. If  $I_3$  is the current in the  $12\Omega$  resistor, and  $I_4$  in the  $6\Omega$  resistor,

$$I_3 \times 12 = I_4 \times 6, \quad \text{i.e., } I_4 = 2I_3$$

$$\text{But, } I_3 + I_4 = I = 2A$$

$$\text{Thus, } I_3 = \left[ \frac{2}{3} A \right], \quad I_4 = \left[ \frac{4}{3} A \right]$$

That is the current in the  $12\Omega$  resistor is  $\frac{2}{3}A$

while the current in the  $6\Omega$  resistor is  $\frac{4}{3}A$ ,

(c) The voltage drops across AB is

$$V_{AB} = I_1 \times 4 = 1A \times 4\Omega = 4V$$

This can also be obtained by multiplying the total current between A and B by equivalent resistance between A and B that is,

$$V_{AB} = 2A \times 2\Omega = 4V$$

The voltage drop across BC is.

$$V_{BC} = 12\Omega \times 1\Omega = 2V$$

Finally, the voltage drop across CD is

$$V_{CD} = 12\Omega \times I_3 = 12\Omega \times \left[\frac{2}{3}\right]A = 8V$$

This can alternatively be obtained by multiplying total current between C and D by the equivalent resistance between C and D that is,  $V_{CD} = 2A \times 4\Omega = 8V$

Note that the total voltage drop across AD is

$$4V + 2V + 8V = 14V$$

Thus the terminal voltage of battery is 14V, while its emf is 16V. The loss of the voltage (=2V) is accounted for the resistance  $1\Omega$  of the battery [ $2A \times 1\Omega = 2V$ ].

**Example 11:** The four arms of Wheatstone bridge (See figure) have the following resistance:

$$AB = 10\Omega, BC = 10\Omega, CD = 5\Omega \text{ and } DA = \Omega$$

A galvanometer of  $15R = 2\Omega + 4\Omega + 1\Omega = 7\Omega$  resistance is connected across BD. Calculate the current through the galvanometer when a potential difference of 10 V is maintained across AC.


**Sol:** Use KVL for current distribution across each component as shown in circuit (see figure) and solve to get current through galvanometer.

Considering the mesh BADB, we have

$$100I_1 + 15I_2 - 60I_2 = 0$$

$$\text{or } 20I_1 + 3I_2 - 12I_2 = 0$$

(a)

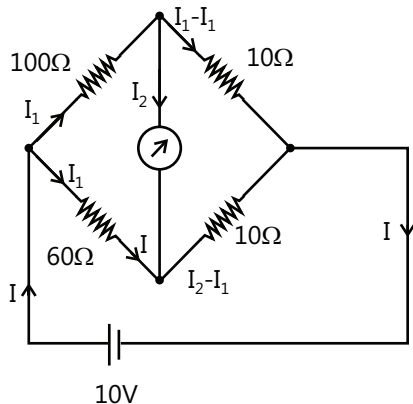

Considering the mesh BCDB. We have

$$10(I_1 + I_g) - 15I_g - 5(I_1 - I_g) = 0$$

$$10I_1 + 30I_g - 5I_2 = 5 \quad ; \quad 20I_1 + 6I_g = I_2 = 0$$

(b) Considering the mesh ADCEA,

$$60I_2 + 5(I_1 - I_g) = 10$$

$$65I_2 + 5I_g = 10 \quad ; \quad 13I_2 + I_g = 2$$

(c) Multiplying Eq. (b) by 10

$$20I_1 + 60I_g - 10I_2 = 0$$

(d) From Eqs. (d) and (a) we have

$$I_2 = 31.5I_g$$

Substituting the value of  $I_2$  into Eq. (c), we get


$$13(31.5I_g) + I_g = 2 \quad ; \quad 410.5 + I_g = 2 \quad ; \quad I_g = 4.87mA$$

**Example 12:** In a meter bridge (See figure), the null point is found at distance of 33.7cm from A. If now a resistance of  $12\Omega$  connected in parallel with S, the null point occurs at 51.9cm. Determine the values of R and S.

**Sol:** for meter bridge  $E \propto \ell \Rightarrow R \propto \ell$

From the first balance point, we get
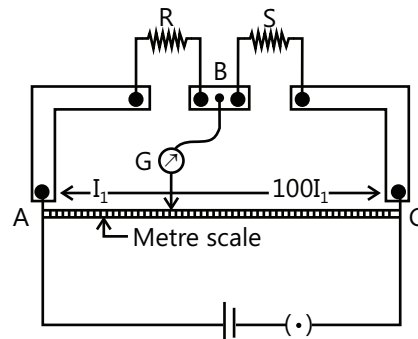
$$\frac{R}{S} = \frac{3}{66.3} \quad \dots(i)$$



After S is connected in parallel with a resistance of  $12\Omega$ , the resistance across the gap changes from S to  $S_{eq}$  where  $S_{eq} = \frac{12S}{S+12}$

$$\text{and hence the new balance condition now gives}$$


$$\frac{51.9}{48.1} = \frac{R(S+12)}{12S} \cdot \frac{33.7}{66.3} \quad \dots(ii)$$

Substituting the value of R/S from Eq. (i), we get

$$\frac{51.9}{48.1} = \frac{R(S+12)}{12S} \cdot \frac{33.7}{66.3}$$


Which gives  $S = 13.5\Omega$ . Using the value of  $R/S$  above, we get  $R = 6.86\Omega$

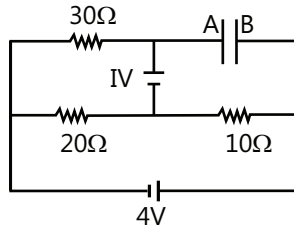**Example 13:** Calculate the potential difference between the plates A and B of the capacitor in adjacent circuit.



**Sol:** Use KVL for current distribution across each component and compute the p.d. across plates A and B.

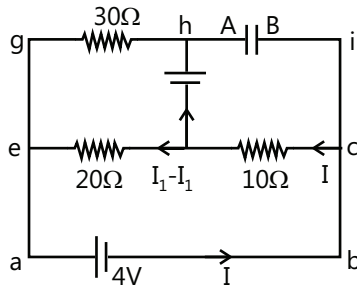The distribution of the current shown in figure. Applying Kirchoff's second Law to the closed loop abedea



We have,

$$= 10I = 20(I - I_1) + 4 = 0 \quad ; \quad \therefore 30I - 20I_1 = 4.$$

For the dhge loop

$$20(I - I_1) + I = 30I_1 = 0 \quad ; \quad \therefore 20I = 50I_1 = -1$$

Solving equation (i) and (ii), we have,

$$I_1 = 0.1\text{A} \quad \text{and} \quad I = 0.2\text{A}.$$

The pd between the two plates of the capacitor is equal to the pd between c and h point. Let  $100I_1 + 15I - 60I_2 = 0$  be the potential at point c and let  $20I_1 + I_g - 21I_2 = 0$  be the potential at h. For the path odh, we have

$$\therefore V_c = 10 \times 0.2 + 1 = V_b$$

$$\therefore V_c = V_a = 2 = 1 + 1$$

$\therefore$  The potential difference between the two capacitor = 1 V


**Example 14:** A potentiometer circuit is shown in the figure, the length of the potentiometer wire is equal to 50 cm  $E_1 = 4\text{V}$ . The internal resistance of the battery can ignored. The values of the resistance  $R_1$  and  $R_2$  are  $15\Omega$  and  $5\Omega$ . The balanced point is obtained at a distance of 31.25 cm from the end A, where both the keys are

open. When both the keys are closed the balanced point is obtained at only 5 cm. Calculate.

(a) The emf of  $E_1$

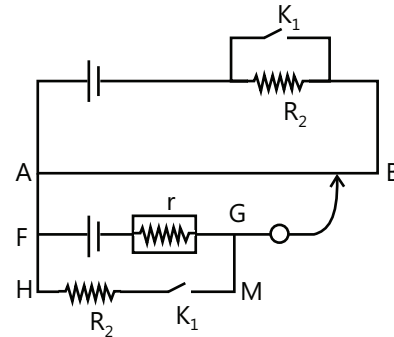(b) The internal resistance of  $E_2$

The resistance of the potentiometer wire  $R_{AB} = 10\Omega$ .



**Sol:** For potentiometer circuit,

$E \propto l$ . Use KVL and solve for the current in the circuit. Use Ohm's law to get internal resistance of cell  $E_2$ .

(a) Resistance  $R_1$  is connected into the circuit when both the keys are open while  $R_2$  gets

Disconnected

$$\varepsilon_1 = 4\text{V} \quad \therefore \varepsilon_2 = \left( \frac{\varepsilon_1 \rho}{R_1 + R_{AB}} \right) I_1$$

$$\rho = \frac{10}{0.5} = 20\Omega\text{m}^{-4}$$

$$R_1 = 15\Omega \quad \therefore \varepsilon_2 = \left( \frac{4 + 20}{5 + 10} \right) 31.25 \times 10^{-2}$$

$$R_{AB} = 10\Omega \quad \therefore \varepsilon_2 = 1\text{V}$$

$$I_2 = 31.25\text{cm} = 31.25 \times 10^{-2}\text{m}$$

(b) Resistance  $R_1$  gets short circuited when both of the keys are closed, in other words resistance  $R_1$  is not connected in the circuit while  $R_2$  gets connected.

Let  $V_{12}$  be the pd between point A and jockey which is equal to the p.d. between points F and G of the circuit.

$$V_{12} = \frac{\varepsilon_1 \times I_2 \times \rho}{R_{AB}} = \frac{4 \times 5 \times 10^{-2} \times 20}{10}$$

$$\therefore V_{12} = 4 \times 10^{-2}\text{V}$$

Now, the pd. between point F and G =  $E_2 - Ir$

Where  $I$  = current flowing through the battery  $E_2$ . It can be seen from the diagram that current does flow from the circuit FHM'G'F, even if the galvanometer shown

zero deflection which means that current flow the  $E_2$  battery which results in a pd between point 'F' and 'G'.

$$E_2 = Ir$$

The pd should be equal to  $V_{12}$  using equation in the above result, we have,

$$40 \times 10^{-2} = \varepsilon_1 = Ir$$

The current flowing in the circuit FHMGG'F' is equal to.

$$I = \frac{\varepsilon_1}{R_2 + r}$$

$$\therefore 40 \times 10^{-2} = \varepsilon_2 - \frac{\varepsilon_2 r}{R_2 + r} = \varepsilon_2 \left[ 1 - \frac{r}{R_2 + r} \right]$$

$$= \varepsilon_2 - \frac{\varepsilon_2 + r - r}{R_2 + r} \therefore 40 \times 10^{-2} = \varepsilon_2 \left[ \frac{R_2}{R_2 + r} \right] = 1 \left[ \frac{5}{5 + r} \right]$$

$$\therefore 5 + r = \frac{5}{40 \times 10^{-2}} = 12.5 \Omega$$


$$\therefore r = 12.5 - 5 = 7.5 \Omega$$

## JEE Advanced/Boards

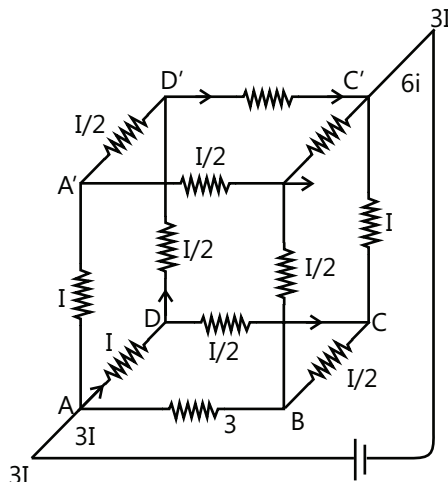**Example 1:** A battery of 10 V and negligible internal resistance is connected across the diagonally opposite corners of a cubical network consisting of 12 resistors each of resistance  $1 \Omega$  (see figure below). Determine the equivalent resistance of the network and the current along each edge of the cube.

**Sol:** Use KVL and for p.d. across each component and solve for current through each component.

The network is not reducible to a simple series and parallel combinations of resistors. There is however, clear symmetry in the problem which we can exploit to obtain the equivalent resistance of the network.



The path AA', AD and AB are obviously symmetrically placed in the network. Thus, the current in each must be same say, I. Further, at the corners A', B and D, the incoming current I must split equally into the two outgoing branches. In this manner, the current in all the 12 edges of the cube are easily written down in terms of I, using Kirchhoff's first rule and the symmetry in the problem. Next take a closed loop, say, ABCC'EA, and apply Kirchhoff's second rule:

$$= IR = (1/2)IR - IR + \varepsilon = 0$$

where R is the resistance of each edge and  $\varepsilon$  the emf of

battery. Thus,  $\varepsilon = \frac{5}{2}IR$

The equivalent  $R_{eq}$  of the network is

$$R_{eq} = \frac{\varepsilon}{3I} = \frac{5}{6}R$$


For  $R = 1 \Omega$ ,  $R_{eq} = (5/6)\Omega$  and for  $\varepsilon = 10V$ , the

total current ( $=3I$ ) in the network is  $3I = 10V/(5/6)\Omega$

$= 12A$ , i.e.,  $I = 4A$

The current flowing in each edge can now be read off from the figure.

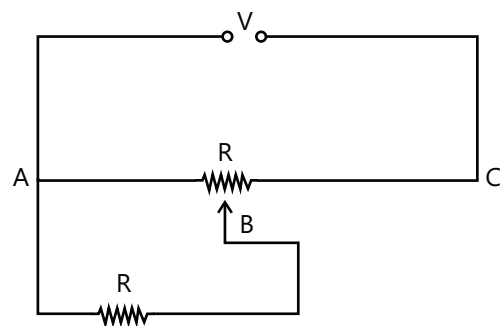**Example 2:** A resistance of  $R \Omega$  draws current from a potentiometer. The potentiometer has a total resistance  $R_0 \Omega$  (see figure). A voltage V is supplied to the potentiometer. Derive an expression for the voltage across R When the sliding contact is in the middle of the potentiometer.



**Sol:** Use formulae for series and parallel combination of resistances. P.D. across each branch is given by Ohm's law.

While the slide is in the middle of the potentiometer only half of its resistance ( $R_0/2$ ) will be between the points A and B. Hence, The total resistance between A and B, say  $R_1$  will be given by the following expression:

$$\frac{1}{R_1} = \frac{1}{R} + \frac{1}{(R_0/2)} ; R_1 = \frac{R_0 R}{R_0 + 2R}$$

The total resistance between A and C will be sum of resistance between A and B and B and C, i.e.  $R_1 + R_0/2$

∴ The current flowing through the potentiometer will be

$$I = \frac{V}{R_1 + R_0/2} = \frac{2V}{2R_1 + R_0}$$

The voltage  $V_1$  taken from the potentiometer will be the product of current  $I$  and resistance  $R_1$ ,


$$V_1 = IR_1 = \left[ \frac{2V}{2R_1 + R_0} \right] \times R_1$$

Substituting for  $R_1$ , we have a

$$V_1 = \frac{2V}{2 \left( \frac{R_0 \times R}{R_0 + 2R} \right) + R_0} \times \frac{R_0 \times R}{R_0 + 2R}$$

$$V_1 = \frac{2VR}{2R + R_0 + 2R} \text{ or } V_1 = \frac{2VR}{R_0 + 4R}$$

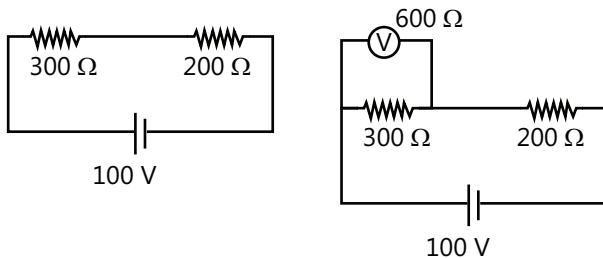**Example 3:** (a) Find the potential drops across the two resistors shown in figure (a). (b) A voltmeter of resistance  $600\Omega$  is used to measure the potential drop across the  $300\Omega$  resistor (see figure (b)). What will be the measured potential drop?



**Sol:** Find the equivalent resistance in both the circuit and then find the p.d. using Ohm's law.

(a) The current in the circuit is  $\frac{100V}{300\Omega + 200\Omega} = 0.2A$

The potential drop across the  $300\Omega$  resistor is  $300\Omega \times 0.2A = 60V$

Similarly, the drop across the  $200\Omega$  resistor is  $40V$ .

(b) The equivalent resistance, when the voltmeter is connected across  $300\Omega$ , is (see figure (b))

$$R = 200\Omega + \frac{600\Omega \times 300\Omega}{600\Omega + 300\Omega} = 400\Omega$$

Thus, the main current from the battery is


$$i = \frac{100V}{400\Omega} = 0.25A$$

The potential drop across the  $200\Omega$  resistance is, therefore,  $200\Omega \times 0.25A = 50V$  and that across  $300\Omega$  is also  $50V$ . This is also the potential drop across the voltmeter and hence the reading of voltmeter is  $50V$ .

**Example 4:** A galvanometer has a coil of resistance  $100\Omega$  showing a full-scale deflection at  $50\mu A$ . What resistance should be added to use it as (a) a voltmeter of range  $50V$  (b) an ammeter of range  $10mA$ ?

**Sol:** To convert galvanometer to voltmeter, connect a large resistance in series with it. To convert galvanometer to ammeter, connect a small resistance in parallel with it. The current through the galvanometer should not exceed its full scale current.

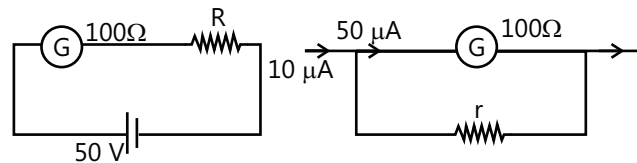(a) When a potential difference of  $50V$  is applied across the voltmeter, full-scale deflection should take place. Thus,  $50\mu A$  should go through the coil. We



add a resistance  $R$  in series with the given coil to achieve this (see figure (a)).

$$\text{We have, } 50\mu A = \frac{50V}{100\Omega + R}$$

$$\text{or } R = 10^6\Omega - 100\Omega \approx 10^6\Omega$$

(b) When a current of  $10mA$  is passed through the ammeter,  $50\mu A$  should go through the coil. We add a resistance  $r$  in parallel to the coil to achieve this (see figure (b)).

The current through the coil is

$$50\mu A = (10mA) \frac{r}{r + 100\Omega} \text{ or } r = 0.5\Omega$$



## JEE Main/Boards

### Exercise 1

**Q.1** The storage battery of a car has an emf of 12V. If the internal resistance of the battery is  $0.4\ \Omega$ , what is the maximum current that can be drawn from the battery?

**Q.2** A battery of emf 10V and internal resistance  $3\ \Omega$  is connected to a resistor. If the current in the circuit is 0.5A, what is the resistance of the resistor? What is the terminal voltage of the battery when the circuit is closed?

**Q.3** (a) Three resistors  $1\ \Omega$ ,  $2\ \Omega$ , and  $3\ \Omega$  are combined in series. What is the total resistance of the combination?

(b) If the combination is connected to a battery of emf 12 V and negligible internal resistance, obtain the potential drop across each resistor.

**Q.4** (a) Three resistors  $2\ \Omega$ ,  $4\ \Omega$  and  $5\ \Omega$  are combined in parallel. What is the total resistance of the combination?

(b) If the combination is connected to battery of emf 20V and negligible internal resistance, determine the current through each resistor, and the total current drawn from the battery

**Q.5** At room temperature ( $27.0^\circ\text{C}$ ) the resistance of a heating element is  $100\ \Omega$ . What is the temperature of the element if the resistance is found to be  $117\ \Omega$ , given that the temperature coefficient of the material of the resistor is  $1.70 \times 10^{-6}\ ^\circ\text{C}^{-1}$ .


**Q.6** A negligibly small current is passed through a wire of length 15m and uniform cross-section  $6.0 \times 10^{-7}\ \text{m}^2$ , and its resistance is measured to be  $5.0\ \Omega$ . What is the resistivity of the material at the temperature of the experiment?

**Q.7** A silver wire has a resistance of  $2.1\ \Omega$  at  $27.5^\circ\text{C}$ , and a resistance of  $2.7\ \Omega$  at  $100^\circ\text{C}$ . Determine the temperature coefficient of resistivity of silver.

**Q.8** A heating element using nichrome connected to a 230V supply drawn an initial current of 3.2A which settles after a few seconds to a steady value of 2.8A. What is the steady temperature of the heating element

if the room temperature is  $27.0^\circ\text{C}$ ? Temperature coefficient of resistance of nichrome averaged over the temperature range involved is  $1.70 \times 10^{-4}\ ^\circ\text{C}^{-1}$ .

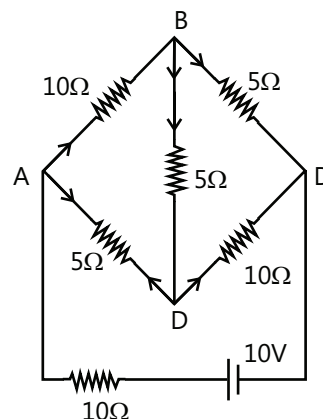**Q.9** Determine the current in each branch of the network shown in figure:



**Q.10** A storage battery of emf 8.0V and internal resistance  $0.5\ \Omega$  is being charged by a 120V DC supply using a series resistor of  $15.5\ \Omega$ . What is the terminal voltage of the battery during charging? What is the purpose of having a series resistor in the charging circuit?

**Q.11** In potentiometer arrangement, a cell of emf 1.25V gives a balance point at 35.0cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63.0cm, what is the emf of the second cell?

**Q.12** The number density of free electrons in a copper conductor as estimated is  $8.5 \times 10^{28}\ \text{m}^{-3}$ . How long does an electron take to drift from one end of a wire 3.0m long to its other end? The area of cross-section of the wire is  $2.0 \times 10^{-6}\ \text{m}^2$  and it is carrying a current of 3.0A.

**Q.13** The earth's surface has a negative surface charge density of  $10^{-9}\ \text{cm}^{-2}$ . The potential difference of 400kV between the top of the atmosphere and the surface results (due to the low conductivity of the lower atmosphere) in a current of only 1800A over the entire globe. If there were no mechanism of sustaining atmospheric electric field, how much time (roughly) would be required to neutralise the earth's surface? (This never happens in practice because there is a

mechanism to replenish electric charges, namely the continual thunderstorms and lighting in different parts of the globe). (Radius of earth =  $6.37 \times 10^6$  m)

**Q.14** (a) Six lead-acid type of secondary cells each of emf 2.0V and internal resistance  $0.015\Omega$  are joined in series to provide a supply to a resistance of  $8.5\Omega$ . What are the current drawn from the supply and its terminal voltage?

(b) A secondary cell after long use has an emf of 1.9V and a large internal resistance of  $380\Omega$ . What maximum current can be drawn from the cell? Could the cell drive the starting motor of a car?

**Q.15** Two wire of equal length, one aluminium and the other of copper have the same resistance. Which of the two wire is lighter? Hence explain why aluminium wires are preferred for overhead power cables.

$$(\rho_{A1} = 2.63 \times 10^{-8} \Omega\text{m}, \rho_{A2} = 1.72 \times 10^{-8} \Omega\text{m},$$

Relative density of Al = 2.7, of Cu = 8.9)

**Q.16** Answer the following questions:

(a) A steady current flow in a metallic conductor of non-uniform cross-section. Which of these quantities is constant along the conductor: current, current density, electric field drift speed?

(b) Is ohm's law universally applicable for all conducting elements? If not, given examples of elements which do not obey ohm's law.

(c) A low voltage supply from which one needs high currents must have very low internal resistance. Why?

(d) A high tension (HT) supply, of say 6kV, must have a very large internal resistance. Why?

**Q.17** Choose the correct alternative:

(a) Alloys of metals usually have (greater/less) resistivity than that of their constituent metals.


(b) Alloys usually have much (lower/higher) temperature coefficients of resistance than pure metals.

(c) The resistance of the alloy manganin (is nearly independent of / increases rapidly with increases of) temperature.


(d) The resistivity of a typical insulator (e.g., amber) is greater than that of a metal by a factor of the order of ( $10^{22}$ / $10^3$ ).

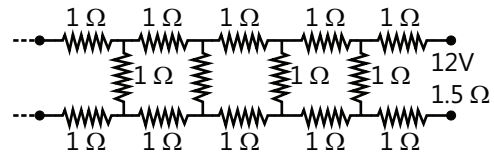**Q.18** Determine the current drawn from a 12V supply

with internal resistance  $0.5\Omega$  by the infinite network shown in figure. Each resistor has  $1\Omega$  resistance.



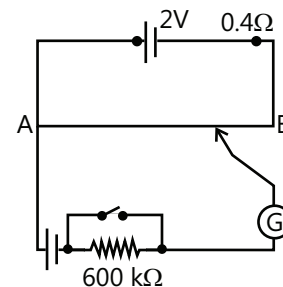**Q.19** Figure shows a potentiometer with a cell of 2.0V and internal resistance  $0.40\Omega$  maintaining a potential drop across the resistor wire AB. A Standard cell which maintains a constant emf of 1.02V (for every moderate up to a few mA) Give a balance point at 63.7cm length of the wire. To ensure very low currents drawn from the standard cell, a very high resistance of  $600\text{k}\Omega$  is put in series with it, which is shorted close to the balance point. The standard cell is then replaced by a cell of unknown emf  $\varepsilon$  and the balance point found similarly, turns out to be at 82.3cm length of the wire.



(a) What is the values  $\varepsilon$ ?

(b) What purpose does the high resistance of  $600\text{ k}\Omega$  have?


(c) Is the balance point affected by this high resistance?

(d) Is the balance point affected by the internal resistance of the driver cell?

(e) Would the method work in the above situation if the driver cell of the potentiometer had an emf 1.0V instead of 2.0V?

(f) Would the circuit work well for determining an extremely small emf, say of the order of a few mV (such as the typical emf of a thermo-couple)? If not, how will you modify the circuit?

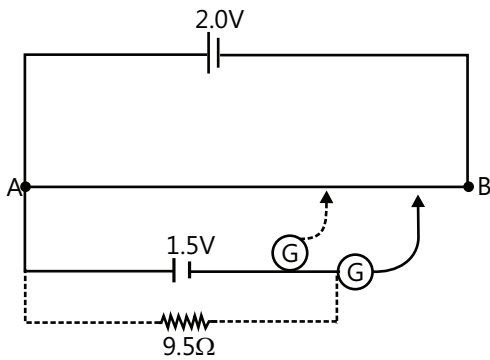**Q.20** Figure shows a 2.0 V potentiometer used for the determining of internal resistance of a 1.5 V cell. The balance point of the cell in open circuit is 76.3cm. When a resistor of  $9.5\text{ W}$  is used in the external circuit of the cell, the balance point shifts to 64.8 cm length of the potentiometer wire. Determine the internal resistance of the cell.



**Q.21** A galvanometer coil has a resistance of  $12\Omega$  and the meter shows full scale deflection for a current of  $3\text{mA}$ . How will you convert the bridge into a voltmeter of range 0 to  $18\text{V}$ ?

**Q.22** A galvanometer coil has resistance of  $15\Omega$  and the meter shows full scale deflection for a current of  $4\text{mA}$ . How will you convert the meter into an ammeter of range 0 to  $6\text{A}$ ?

**Q.23** A  $10\text{m}$  long wire of uniform cross-section of  $20\Omega$  resistance is fitted in a potentiometer. This wire is connected in series with a battery of  $5\text{V}$ , along with an external resistance of  $480\Omega$ . If an unknown emf  $E$  is balanced at  $6.0\text{m}$  length of this wire, calculate (i) the potential gradient of the potentiometer wire, (ii) the value of the unknown emf  $E$ .

**Q.24** (a) Three cells of emf  $2.0\text{V}$ ,  $1.8\text{V}$ , and  $1.5\text{V}$  are connected in series. Their internal resistances are  $0.05\Omega$ ,  $0.7\Omega$  and  $1\Omega$ , respectively. If the battery is connected to an external resistor of  $4\Omega$  via a very low resistance ammeter, what would be the reading in the ammeter?



(b) If the three cells above were joined in parallel, would they be characterized by a definite and internal resistance (independent of external circuit)? If not, how will you obtain currents in different branches of the circuit?

**Q.25** A galvanometer with a coil of resistance  $12.0\Omega$  shows a full scale deflection for a current of  $2.5\text{mA}$ . How will you convert the galvanometer into (a) an ammeter of range 0 to  $7.5\text{A}$ , (b) a voltmeter of range 0 to  $10.0\text{V}$ . Determine the net resistance of the meter in each case. When an ammeter is put in a circuit, does it read (slightly) less or more than the actual current in the original circuit? When a voltmeter is put a cross a part of circuit, does it read (slightly) less or more than the original voltage drop? Explain.

**Q.26** With two resistance  $R_1$  and  $R_2$  ( $> R_1$ ) in the two gaps of a meter bridge, the balance point was found to be  $\frac{1}{3}$  m from the zero end. When a  $6\Omega$  resistance is connected in series with the smaller of the two resistance, the point is shifted to  $\frac{2}{3}$  m from the same end. Calculate  $R_1$  and  $R_2$ .

**Q.27** A set of 4 cells, each of emf  $2\text{V}$  and internal resistance  $1.05\Omega$ , are connected across an external load of  $10\Omega$ . with 2 rows, 2 cells in each branch. Calculate the current in each branch and potential difference across  $10\Omega$ .

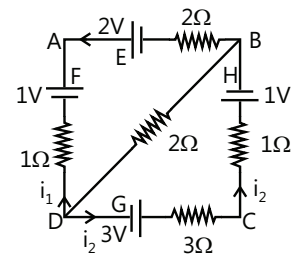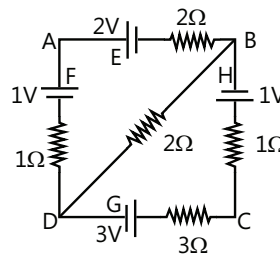**Q.28** In the circuit shown in figure E,F,G and H are cells of emf  $2,1,3$  and  $1\text{V}$  respectively. The resistances  $2,1,3$  and  $1\Omega$  are their respective internal resistance. Calculate (a) the potential difference between B and D and (b) the potential difference across the terminals of each of the cells G and H.




## Exercise 2

**Q.1** A current  $I$  flow through a uniform wire of diameter  $d$  when the mean electron drift velocity is  $V$ . The same current will flow through a wire of diameter  $d/2$  made of the same material if the mean drift velocity of the electron is:

- (A)  $V/4$  (B)  $V/2$  (C)  $2V$  (D)  $4V$

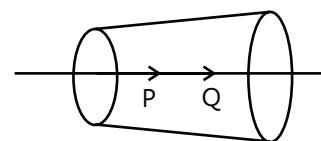**Q.2** A wire has a non- uniform cross- section as shown in figure. A steady current flows through it. The drift speed of electrons at point p and q is  $V_p$  and  $V_q$ .




- (A)  $V_p = V_q$  (B)  $V_p < V_q$   
(C)  $V_p > V_q$  (D) Data insufficient

**Q.3** A uniform copper wire carries a current  $i$  amperes and has  $p$  carriers per cubic meter. The length of the wire is  $l$  meters and its cross-section area is  $s$  meter<sup>2</sup>. If the charge on a carrier is  $q$  coulombs, the drift velocity in  $\text{ms}^{-1}$  is given by


- (A)  $i/ps$       (B)  $i/psq$       (C)  $psq/i$       (D)  $i/pslq$

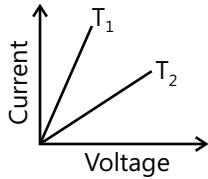**Q.4** The current in a metallic conductor is plotted against voltage at two different temperatures  $T_1$  and  $T_2$ . Which is correct




- (A)  $T_1 > T_2$       (B)  $T_1 < T_2$   
 (C)  $T_1 = T_2$       (D) None of these

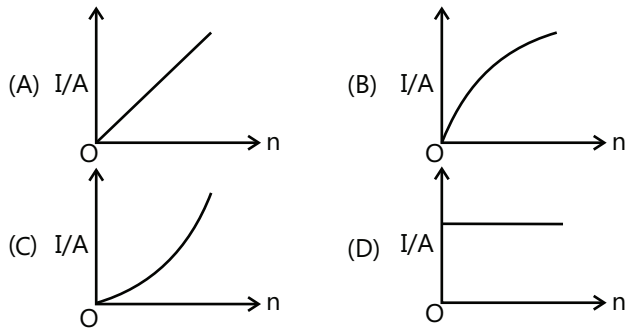**Q.5** A battery consists of a variable number  $n$  of identical cells having internal resistance connected in series. The terminal of the battery are short circuited and the current  $I$  measured. Which one of the graph below shows the relationship between  $I$  and  $n$ ?




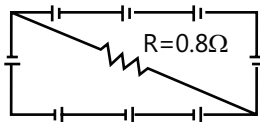**Q.6** A circuit is comprised of eight identical batteries and a resistor  $R = 0.8\Omega$ . Each battery has an emf  $1.0\text{V}$  and internal resistance of  $0.2\Omega$ . The voltage difference across any of the battery is




- (A)  $0.5\text{V}$       (B)  $1.0\text{V}$       (C)  $0\text{V}$       (D)  $2\text{V}$

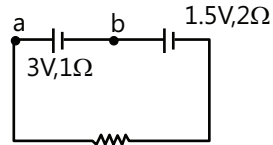**Q.7** Two batteries one of the emf  $3\text{V}$ , internal resistance  $1\text{ohm}$  and the other of emf  $15\text{V}$ , internal resistance  $2\text{ohm}$  are connected in series with a resistance  $R$  as shown. If the potential difference between  $a$  and  $b$  is zero the resistance of  $R$  in ohm is



- (A)  $5$       (B)  $7$       (C)  $3$       (D)  $1$

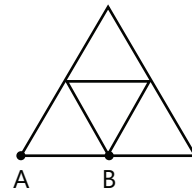**Q.8** In the diagram resistance between any two junctions is  $R$ . Equivalent resistance across terminals  $A$  and  $B$  is



- (A)  $\frac{11R}{7}$       (B)  $\frac{18R}{11}$       (C)  $\frac{7R}{11}$       (D)  $\frac{11R}{18}$


**Q.9** When electric bulbs of same power, but different marked voltage are connected in series across the power line, their brightness will be:


- (A) Proportional to their marked voltage  
 (B) Inversely proportional to their marked voltage  
 (C) Proportional to the square of their marked voltage  
 (D) Inversely proportional to the square of their marked voltage

**Q.10** Two bulbs rated  $(25\text{W} - 220\text{V})$  and  $(100\text{W} - 220\text{V})$  are connected in series to a  $440\text{V}$  line. Which one is likely to fuse?


- (A)  $25\text{W}$  bulb      (B)  $100\text{W}$  bulb  
 (C) Both bulbs      (D) None

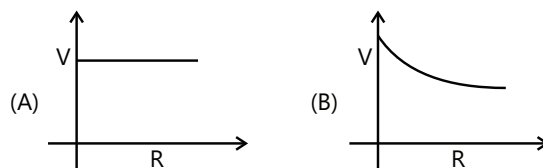**Q.11** A cell of emf  $E$  has an internal resistance  $r$  & is connected to rheostat. When resistance  $R$  of rheostat is changed correct graph of potential across it is (see figure)



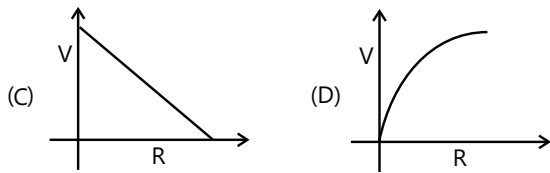

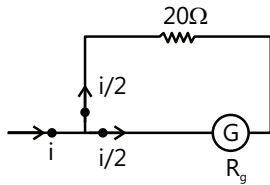**Q.12** The battery in the diagram is to be charged by the generator G. The generator has a terminal voltage of 120 volts when the charging current is 10 amperes. The battery has an emf of 100 volts and an internal resistance of 1 ohm. In order to charge the battery at 10 amperes charging current, the resistance R should be set at



- (A) 0.1  $\Omega$     (B) 0.5  $\Omega$     (C) 1.0  $\Omega$     (D) 5.0  $\Omega$

**Q.13** In a galvanometer, the deflection becomes one half when the galvanometer is shunted by a  $20\Omega$  resistor. The galvanometer resistance is

- (A) 5  $\Omega$     (B) 10  $\Omega$     (C) 40  $\Omega$     (D) 20  $\Omega$


**Q.14** A galvanometer has a resistance of  $20\Omega$  and reads full-scale when 0.2 V is applied across it. To convert it into a 10 A ammeter, the galvanometer coil should have a

- (A)  $0.01\Omega$  resistor connected across it  
 (B)  $0.02\Omega$  resistor connected across it  
 (C)  $200\Omega$  resistor connected in series with it  
 (D)  $2000\Omega$  resistor connected in series with it

**Q.15** A galvanometer coil has a resistance  $90\Omega$  and full scale deflection current 10 mA. A  $910\Omega$  resistance is connected in series with the galvanometer to make a voltmeter. If the least count of the voltmeter is 0.1V, the number of divisions on its scale is


- (A) 90    (B) 91    (C) 100    (D) None

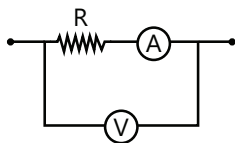**Q.16** In the circuit shown the resistance of voltmeter is 10,000 ohm and that of ammeter is 20 ohm. The ammeter reading is 0.10 Amp and voltmeter reading is 12 volt. Then R is equal to



- (A) 122  $\Omega$     (B) 140  $\Omega$     (C) 116  $\Omega$     (D) 100  $\Omega$

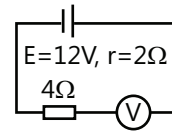**Q.17** By error, a student place moving-coil voltmeter V (nearly ideal) in series with the resistance in a circuit in order to read the current, as shown (see figure). The voltmeter reading will be



- (A) 0    (B) 4 V    (C) 6 V    (D) 12 V


**Q.18 Statement-I:** Conductivity of a metallic conductor decreases with increases in temperature.

**Statement-II:** On increasing temperature the number of free electrons in the metallic conductor decreases.

- (A) Statement-I is true, statement-II is true and statement-II is correct explanation for statement-I.  
 (B) Statement-I is true, statement-II is true and statement-II is NOT the correct explanation for statement-I  
 (C) Statement-I is true, statement-II is false.  
 (D) Statement-I is false, statement-II is true.

## Previous Years' Questions

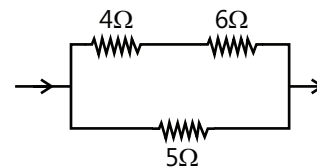
**Q.1** In the circuit shown in figure the heat produced the  $5\Omega$  resistor due to the current flowing through it is 10 cal/s. (1981)



The heat generated in the  $4\Omega$  resistor is


- (A) 1 cal/s    (B) 2 cal/s  
 (C) 3 cal/s    (D) 4 cal/s

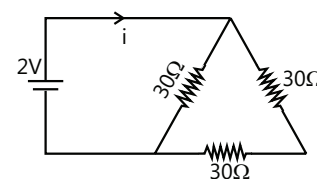**Q.2** The current i in the circuit (see figure) is




- (A)  $\frac{1}{45}$  A    (B)  $\frac{1}{15}$  A    (C)  $\frac{1}{10}$  A    (D)  $\frac{1}{5}$  A

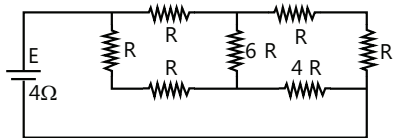**Q.3** A battery of internal resistance  $4\Omega$  is connected to the network of resistances as shown in figure. In order that the maximum power can be delivered to the network, the value of  $R$  in  $\Omega$  should be. **(1995)**




- (A)  $\frac{4}{9}$       (B) 2      (C)  $\frac{8}{3}$       (D) 18

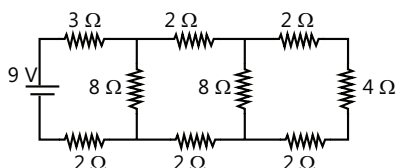**Q.4** In the circuit shown in the figure, the current through **(1998)**




- (A) The  $3\Omega$  resistor is 0.50A  
 (B) The  $3\Omega$  resistor is 0.25A  
 (C) The  $4\Omega$  resistor is 0.50A  
 (D) The  $4\Omega$  resistor is 0.25A

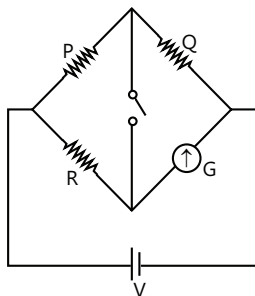**Q.5** In the circuit shown  $P \neq R$ , the reading of galvanometer is same with switch  $S$  open or closed. Then **(1999)**



- (A)  $I_R = I_G$       (B)  $I_P = I_G$       (C)  $I_Q = I_G$       (D)  $I_S = I_G$

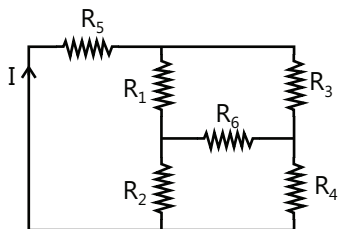**Q.6** In the given circuit, it is observed that the current  $I$  is independent of the value of the resistance  $R_6$ . Then, the resistance values must satisfy **(2001)**



(A)  $R_1 R_2 R_5 = R_3 R_4 R_6$

(B)  $\frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$


(C)  $R_1 R_4 = R_2 R_3$

(D)  $R_1 R_3 = R_2 R_4$

**Q.7** A wire of length  $L$  and 3 identical cells of negligible internal resistance are connected in series. Due to the current, the temperature of the wire is raised by  $\Delta T$  in a time  $t$ . A number  $N$  of similar cells is now connected in series with a wire of the same material and cross-section but of length  $2L$ . The temperature of the wire is raised by the same amount  $\Delta T$  in the time. The value of  $N$  is **(2001)**


- (A) 4      (B) 6      (C) 8      (D) 9

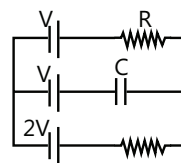**Q.8** In the given circuit, with steady current, the potential difference across the capacitor must be **(2001)**



- (A)  $V$       (B)  $V/2$       (C)  $V/3$       (D)  $2V/3$

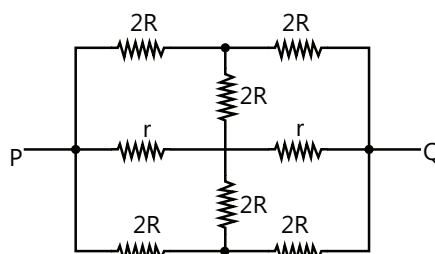
**Q.9** The effective resistance between point  $P$  and  $Q$  of the electrical circuit shown in the figure is **(2002)**




(A)  $\frac{2Rr}{R+r}$       (B)  $\frac{8R(R+r)}{3R+r}$

(C)  $2r + 4R$       (D)  $\frac{5R}{2} + 2r$




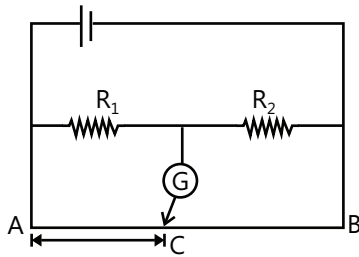
**Q.10** In shown arrangement of the experiment of the meter bridge if  $AC$  corresponding to null deflection of galvanometer is  $x$ , what would be its value if the radius of the wire  $AB$  is doubled? **(2003)**



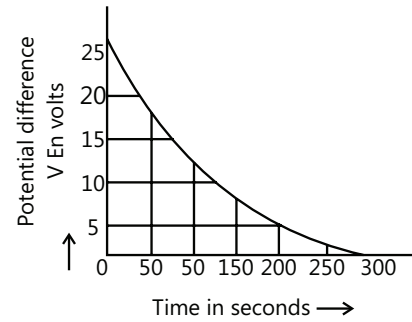- (A)  $x$       (B)  $x/4$       (C)  $4x$       (D)  $2x$



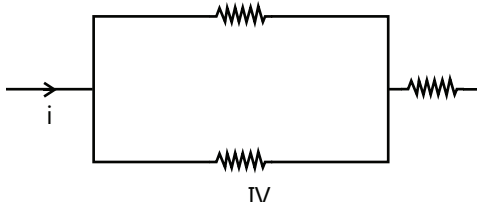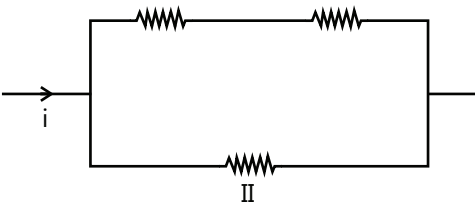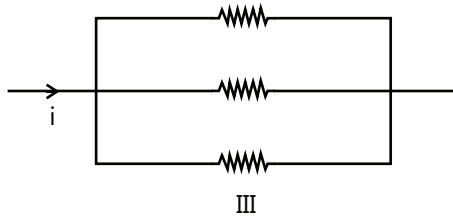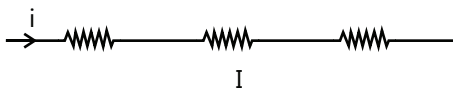**Q.11** The three resistance of equal value are arranged in the different combinations shown below. Arrange them in increasing order of power dissipation (2003)



- (A) III < II < IV < I      (B) II < III < IV < I  
 (C) I < IV < III < II      (D) I < III < II < IV

**Q.12** The figure shows an experimental plot for discharging of a capacitor in an R-C circuit. The time constant  $\tau$  of this circuit lies between : (2012)


- (A) 150 sec and 200 sec  
 (B) 0 and 50 sec  
 (C) 50 sec and 100 sec  
 (D) 100 sec and 150 sec

**Q.13** The electric bulbs marked 25 W – 220 V and 100 W – 220 V are connected in series to a 440 V supply. Which of the bulbs will fuse ? (2012)

- (A) Both      (B) 100 W  
 (C) 25 W      (D) Neither

**Q.14** The supply voltage to a room is 120 V. The resistance of the lead wires is  $6\ \Omega$ . A 60 W bulb is already switched on. What is the decrease of voltage across the bulb, when a 240 W heater is switched on in parallel to the bulb ? (2013)

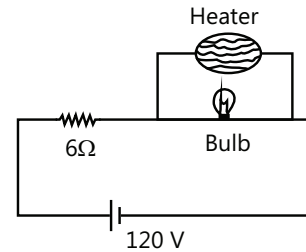- (A) 2.9 Volt      (B) 13.3 Volt  
 (C) 10.04 Volt      (D) Zero volt



**Q.15** This question has statement-I and statement-II. Of the four choices given after the statements, choose the one that best describes the two statement.

Statement-I: Higher the range, greater is the resistance of ammeter.

Statement-II: To increase the range of ammeter, additional shunt needs to be used across it. (2013)


- (A) Statement-I is true, statement-II is true, statement-II is not the correct explanation of statement-I  
 (B) Statement-I is true, statement-II is false  
 (C) Statement-I is false, statement-II is true  
 (D) Statement-I is true, statement-II is true, statement-II is the correct explanation of statement-I

**Q.16** In a large building, there are 15 bulbs of 40 W, 5 bulbs of 100 W, 5 fans of 80 W and 1 heater of 1kW. The voltage of the electric mains is 220 V. The minimum capacity of the main fuse of the building will be: **(2014)**

- (A) 12 A      (B) 14 A      (C) 8 A      (D) 10 A

**Q.17** In the circuit shown, the current in the  $1\ \Omega$  resistor is: **(2015)**

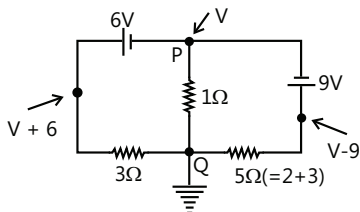- (A) 0 A  
 (B) 0.13 A, from Q to P  
 (C) 0.13 A, from P to Q  
 (D) 1.3 A, from P to Q



**Q.18** When 5V potential difference is applied across a wire of length 0.1 m, the drift speed of electrons is  $2.5 \times 10^{-4}\ \text{ms}^{-1}$ . If the electron density in the wire is  $8 \times 10^{28}\ \text{ms}^{-3}$ , the resistivity of the material is close to: **(2015)**

- (A)  $1.6 \times 10^{-7}\ \Omega\text{m}$       (B)  $1.6 \times 10^{-6}\ \Omega\text{m}$   
 (C)  $1.6 \times 10^{-5}\ \Omega\text{m}$       (D)  $1.6 \times 10^{-8}\ \Omega\text{m}$


**Q.19** A galvanometer having a coil resistance of  $100\ \Omega$  gives a full scale deflection, when a current of 1 mA is passed through it. The value of the resistance, which can convert this galvanometer into ammeter giving a full scale deflection for a current of 10 A is: **(2016)**

- (A)  $2\ \Omega$       (B)  $0.1\ \Omega$       (C)  $3\ \Omega$       (D)  $0.01\ \Omega$


## JEE Advanced/Boards

### Exercise 1

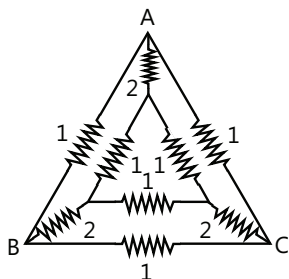
**Q.1** A network of nine conductors connects six point A, B, C, D, E and F as shown in figure. The figure denotes resistances in ohms. Find the equivalent resistance between A and D.



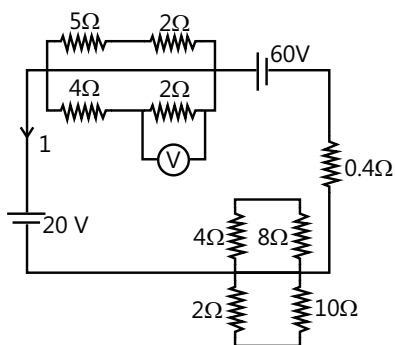
**Q.2** Find the current I & voltage V in the circuit shown.



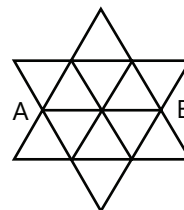**Q.3** Find the equivalent resistance of the circuit between points A and B shown in figure is: (each branch is of resistance =  $1\ \Omega$ )



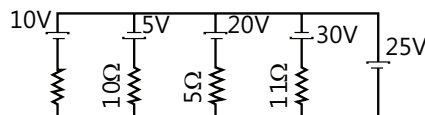
**Q.4** Find the current through 25V cell & power supplied by 20V cell in the figure.




**Q.5** In a cell of constant E.M.F. produces the same amount of the heat during the same time in two independent resistor  $R_1$  and  $R_2$ , when they are separately connected across the terminals of the cell, one after the another, find the internal resistance of the cell.



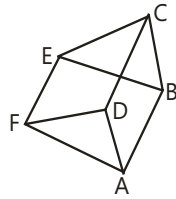
**Q.6** In the circuit shown in figure, all wires have equal resistance  $r$ . Find the equivalent resistance between A and B.



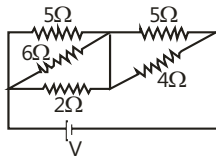
**Q.7** Find the resistor in which maximum heat will be produced.



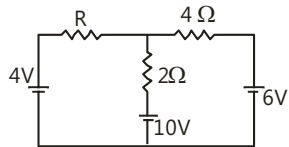
**Q.8** For what value of  $R$  in circuit, current through  $4\Omega$  resistance is zero.



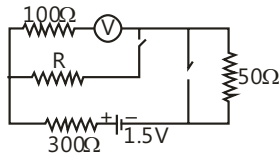
**Q.9** In the circuit shown in figure, the reading of ammeter is the same with both switches open as with both closed. Then find the resistance  $R$ . (ammeter is ideal)



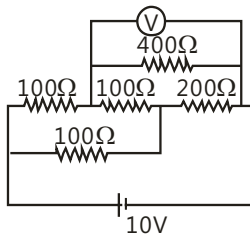
**Q.10** An electrical circuit is shown in the figure. Calculate the potential difference across the resistance of  $400\text{ ohm}$ , as will be measured by the voltmeter  $V$  of resistance  $400\text{ ohm}$ , either by applying Kirchhoff's rules or otherwise.



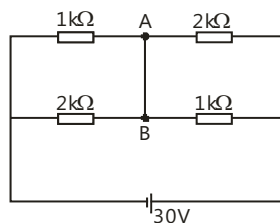
**Q.11** Find the current (in mA) in the wire between points A and B.



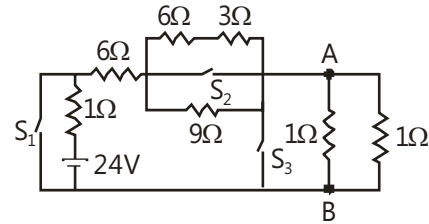
**Q.12** If switches  $S_1, S_2$  and  $S_3$  in the figure are arranged such that current through the battery is minimum, find the voltage across points A and B.



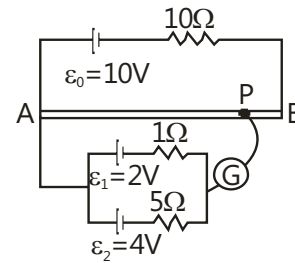
**Q.13** A battery of emf  $e_0 = 10\text{V}$  is connected across a  $1\text{ m}$  long uniform wire having  $10\Omega/\text{m}$ . Two cells of emf  $\epsilon_1 = 2\text{V}$  and  $\epsilon_2 = 4\text{V}$  having internal resistances  $1\Omega$  and  $5\Omega$  respectively are connected as shown in the figure. If a galvanometer shown no deflection at the point P, find the distance of point P from the point a.



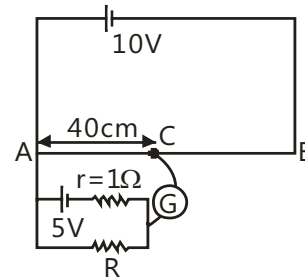
**Q.14** Potentiometer wire AB is  $100\text{ cm}$  long and has a total resistance of  $10\text{ ohm}$ . If the galvanometer shows zero deflection at the position C, then find the value of unknown resistance  $R$ .



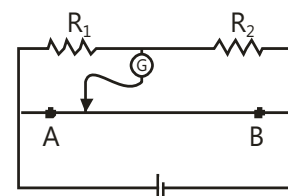**Q.15** In the figure for which value of  $R_1$  and  $R_2$  the balance point for Jockey is at  $40\text{ cm}$  from A. When  $R_2$  is shunted by a resistance of  $10\Omega$ , balance shifts to  $50\text{ cm}$ . Find  $R_1$  and  $R_2$  ( $AB = 1\text{ m}$ ):



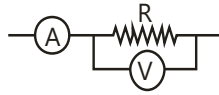**Q.16** A part of a circuit is shown in figure. Here reading of ammeter is 5 ampere and voltmeter is 96 V and voltmeter resistance is 480 ohm. The find the resistance R




**Q.17** A accumulator of emf 2 Volt and negligible internal resistance is connected across a uniform wire of length 10 m and resistance  $30\Omega$ . The appropriate terminals of a cell of emf 1.5 Volt and internal resistance  $1\Omega$  is connected of one end of the wire, and other terminal of the cell is connected through sensitive galvanometer to a slider on the wire. What length of the wire will be required to produce zero deflection of the galvanometer?

How will the balancing change (a) when a coil of resistance  $5\Omega$  is placed series with the accumulator, (b) the cell of 1.5 volt is shunted with  $5\Omega$  resistor?

**Q.18** (a) The current density across a cylindrical conductor of radius R varies according to the equation,  $J = J_0 \left(1 - \frac{r}{R}\right)$  where r is the distance from

the axis. Thus the current density is a maximum  $J_0$  at the axis  $r = 0$  and decreases linearly to zero at the surface  $r = R$ . Calculate the current in terms of  $J_0$  and conductor's cross sectional area is  $A = \pi R^2$ . (b) Suppose that instead the current density is a maximum  $J_0$  at the surface and decreases linearly to zero at the axis so that  $J = J_0 \frac{r}{R}$ . Calculate the current.

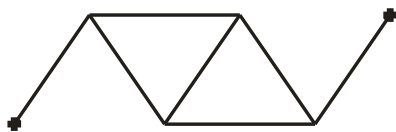
**Q.19** What will be the change in the resistance of a circuit consisting of five identical conductors if two similar conductors are added as shown by the dashed line in figure.



**Q.20** The current I though a rod of a certain metallic oxide is given by  $I = 2V^{5/2}$ , where V is the potential difference across it. The rod is connected in series with a resistance to a 6V battery of negligible internal resistance. What value should the series resistance have so that:

- (i) The current in the current is 0.44
- (ii) The power dissipated in the rod is twice that dissipated in the resistance.

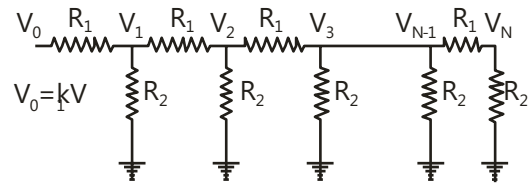
**Q.21** A network of resistance is constructed with  $R_1$  and  $R_2$  as shown in the figure. The potential at the point 1,2,3,..., N are  $V_1, V_2, V_3, \dots, V_n$  respectively each having a potential k time smaller than previous one. Find:



- (i)  $\frac{R_1}{R_2}$  and  $\frac{R_2}{R_3}$  in terms of k
- (ii) Current that passes through the resistance  $R_2$  nearest to the  $V_0$  in terms  $V_0, k$  &  $R_3$ .

**Q.22** A person decides to use his bath tub water to generate electric power to run a 40 watt bulb. The bath tube is located at a height of 10 m from the ground & it holds 200 liters of water. If we install a water driven wheel generator on the ground, at what rate should the water drain from the bath tube to light bulb? How long can we keep the bulb on, if the bath tub was full initially. The efficiency of generator is 90%. ( $g = 10 \text{ m/s}^2$ )

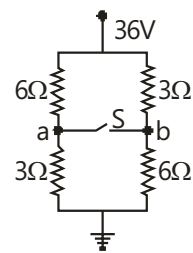**Q.23** In the circuit shown in figure, calculate the following:



- (i) Potential difference between point a and b when switch S is open
- (ii) Current through S in the circuit when S is closed.

**Q.24** A rod length L and cross-section area A lies along the x-axis between  $x = 0$  and  $x = L$ . The material obeys Ohm's law and its resistivity varies along the rod according to  $\rho(x) = \rho_0 e_{x/L}$ . The end of rod at  $x = 0$  is at a potential  $V_0$  and it is zero at  $x = L$ .

- (a) Find the total resistance of the rod and the current in the wire.
- (b) Find the electric potential in the rod as a function of x.

**Q.25** An ideal cell having a steady emf of 2 volt is connected across the potentiometer wire of length 10 m. The potentiometer wire of magnesium and having resistance of  $11.5\Omega/\text{m}$ . An another cell gives a null point at 6.9 m. If a resistance of  $5\Omega$  is put in series with potentiometer wire, find the new position of the null point.


## Exercise 2

### Single Correct Choice Type

**Q.1** An insulating pipe of cross-section area 'A' contains an electrolyte which has two types of ions  $\rightarrow$  their charge begin-e and +2 e. A potential difference applied between the ends of the pipe result in the drifting of the two types of ions, having drift speed = v (-v e ion) and v/4 (+v e ion). Both ions have the same number per unit volume = n. The current flowing through the pipe is

- (A)  $nev A/2$                       (B)  $nev A/4$   
 (C)  $5nev A/2$                       (D)  $3nev A/2$

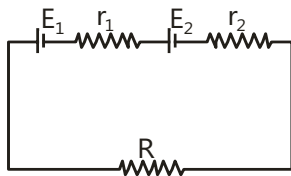**Q.2** Under what condition current passing through the resistance R can be increased by short circuiting the battery of emf  $E_2$ . The internal resistance of the two batteries are  $r_1$  and  $r_2$  respectively.




- (A)  $E_2 r_1 > E_1 (R + r_2)$       (B)  $E_1 r_2 > E_2 (R + r_1)$   
 (C)  $E_2 r_2 > E_1 (R + r_2)$       (D)  $E_1 r_1 > E_2 (R + r_1)$

**Q.3** A wire of length L and 3 identical cells of negligible internal resistance are connected in series. Due to the current, the temperature of the wire is raised by  $\Delta T$  in time t. N number of similar cells is now connected in series with a wire of the same material and cross section but of length 2L. The temperature of the wire is raised by the same amount  $\Delta T$  in the same time t. The value of N is:


- (A) 4                      (B) 6                      (C) 8                      (D) 9

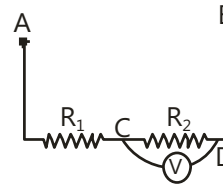**Q.4** Resistance  $R_1$  and  $R_2$  each  $60\Omega$  are connected in series as shown in figure. The Potential difference between A and B is kept 120 volt. Then what will be the reading of voltmeter connected between the point C and D if resistance of voltmeter is  $120\Omega$ .




- (A) 48V                      (B) 24V  
 (C) 40V                      (D) None of these

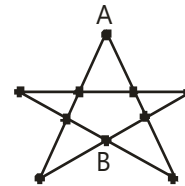**Q.5** The resistance of all the wires between any two adjacent dots is R. The equivalent resistance between A and B as shown in figure is:



- (A)  $7/3 R$                       (B)  $7/6 R$   
 (C)  $14/8 R$                       (D) None of these

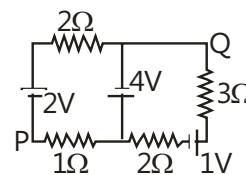**Q.6** In the circuit shown, what is the potential difference  $V_{PQ}$ ?



- (A) +3V                      (B) +2V  
 (C) -2V                      (D) None of these

**Q.7** One end of a Nichrome wire of length 2L and cross-sectional area A is attached to an end of another Nichrome wire of length L and cross-sectional area 2A. If the free end of the longer wire is at an electric potential of 8.0 volt, and the free end of the shorter wire is at an electric potential of 1.0 volt, the potential at the junction of the two wire is equal to


- (A) 2.4 V                      (B) 3.2 V                      (C) 4.5 V                      (D) 5.6 V

**Q.8** Rate of dissipation Joule's heat in resistance per unit volume (Symbols have usual meaning)

- (A)  $\sigma E$  (B)  $\sigma J$  (C)  $JE$  (D) None of these

**Q.9** A millimetre of range 10 mA and resistance  $9\Omega$  is joined in a circuit as shown (see figure). The meter gives full-scale deflection for current  $I$  when A and B are used as its terminals, i.e. current enters leaves at A and leaves at B (C is left isolated). The value of  $I$  is

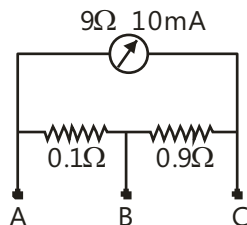
- (A) 100 mA (B) 900 mA  
(C) 1 A (D) 1.1 A



**Q.10** In a balance Wheatstone bridge, current in the galvanometer is zero. It remains when:

- (i) Battery emf is increased  
(ii) All resistance are increased by 10 ohms  
(iii) All resistance are made five times  
(iv) The battery and the galvanometer are interchanged  
(A) Only (i) is correct  
(B) (i), (ii) and (iii) are correct  
(C) (i), (iii) and (iv) are correct  
(D) (i) and (iii) are correct

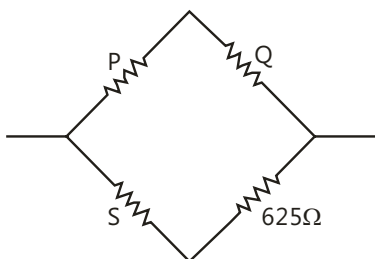**Q.11** A Wheatstone's bridge is balanced with a resistance of  $625\Omega$  in the third arm, where P, Q and S are in the 1<sup>st</sup>, 2<sup>nd</sup> and 4<sup>th</sup> arm respectively. If P and Q are interchanged, the resistance in the third arm has to be increased by  $51\Omega$  to secure balance. The unknown resistance in the fourth arm is




- (A)  $625\Omega$  (B)  $650\Omega$  (C)  $676\Omega$  (D)  $600\Omega$

**Q.12** Which of the following quantities do not change when an ohmic resistor connected to a battery is heated due to the current?


- (A) Drift speed (B) Resistivity  
(C) Resistance (D) Number of free electrons

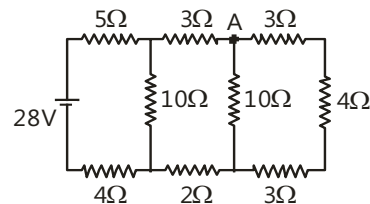**Q.13** Consider the circuit shown in the figure.



- (A) The current in the  $5\Omega$  resistor is 2 A  
(B) The current in the  $5\Omega$  resistor 1 A  
(C) The potential difference  $V_A - V_B$  is a 10V  
(D) The potential difference  $V_A - V_B$  is 5V

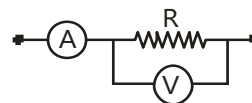
**Q.14** In the circuit shown the readings of ammeter and voltmeter are 4A and 20V respectively. The meters are non-ideal, then R is:



- (A)  $5\Omega$   
(B) Less than  $5\Omega$   
(C) Greater than  $5\Omega$   
(D) Between  $4\Omega$  and  $5\Omega$


### Multiple Correct Choice Type

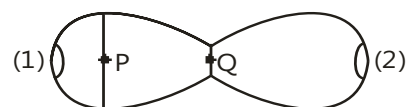**Q.15** A metallic conductor of irregular cross-section is as shown in the figure. A constant potential difference is applied across the ends (1) and (2). Then:



- (A) The current at the cross-section P equals the current at cross-section Q  
(B) The electric field intensity at P is less than that at Q.  
(C) The rate of heat generated per unit time at Q is greater than that at P  
(D) The number of electrons crossing per unit area of cross-section at P is less than that at Q.

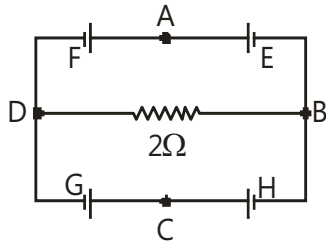**Q.16** In the circuit shown E, F, G and H are cells of e.m.f 2V, 1V, 3V and 1V respectively and their internal resistance are  $2\ \Omega$ ,  $1\ \Omega$ ,  $3\ \Omega$  and  $1\ \Omega$  respectively.



- (A)  $V_D - V_B = -2/13V$   
 (B)  $V_D - V_B = 2/13V$   
 (C)  $V_G = -21/13V =$ potential difference across G.  
 (D)  $V_H = 19/13V =$ potential difference across H.

**Q.17** A micrometre has a resistance of  $100\ \Omega$  and a full scale range of  $50\ \mu A$ . It can be used as a voltmeter or a higher range ammeter provided a resistance is added to it. Pick the correct range and resistance combination (s)

- (A) 50V range with  $10k\ \Omega$  resistance in series.  
 (B) 10V range with  $200k\ \Omega$  resistance in series.  
 (C) 5mA range with  $1\ \Omega$  resistance in parallel  
 (D) 10mA range with  $1k\ \Omega$  resistance in parallel.

**Q.18** In a potentiometer wire experiment the emf of a battery in the primary circuit is 20V and its internal resistance is  $5\ \Omega$ . There is resistance box in series with the battery and the potentiometer wire, whose resistance can be varied from  $120\ \Omega$  to  $170\ \Omega$ . Resistance of the potentiometer wire is  $75\ \Omega$ . The following potential difference can be measured using this potentiometer.

- (A) 5 V      (B) 6V      (C) 7V      (D) 8 V

**Q.19** A current passes through an ohmic conductor of non-uniform cross-section. Which of the following quantities are independent of the cross- section?

- (A) The charge crossing in a given time interval.  
 (B) Drift speed  
 (C) Current density  
 (D) Free-electron density

**Q.20** Mark out the correct options.

- (A) An ammeter should have small resistance  
 (B) An ammeter should have large resistance  
 (C) A voltage should have small resistance  
 (D) A voltage should have large resistance

### Assertion Reasoning Type

- (A) Statement-I is true, statement-II is true and statement-II is correct explanation for statement-I.  
 (B) Statement-I is true, statement-II is true and statement-II is NOT the correct explanation for statement-I  
 (C) Statement-I is true, statement-II is false.  
 (D) Statement-I is false, statement-II is true

**Q.21 Statement-I:** When two conduction wires of different resistivity having same cross section area are joined in series, the electric field in them would be equal when they carry current.

**Statement-II:** When wires are in series they carry equal current.

**Q.22 Statement-I:** potential difference across the terminals of a battery is always less than its emf .

**Statement-II:** A battery always has some internal resistance.

**Q.23 Statement-I:** Knowing that rating is done at steady of the filament, an electric bulb connected to a source having rated voltage consumes more than rated power just after it is switched on.

**Statement-II:** When filament is at room temperature its resistance is less than its resistance when the bulb is fully illuminated.

### Comprehension Type

**Paragraph 1:** Two persons are pulling a square of side  $a$  along one of the diagonals horizontally to make it rhombus. Plane of rhombus is always vertical and uniform magnetic field  $B$  exist perpendicular to plane. They start pulling at  $t = 0$  and with constant velocity  $v$ .

**Q.24** The induced emf in the frame when angle at corner being pulled is  $60^\circ$

- (A)  $Bav$       (B)  $2Bav$       (C)  $\frac{Bav}{2}$       (D)  $\frac{Bav}{4}$

**Q.25** If the resistance of the frame is  $R$  the current induced is

- (A)  $\frac{Bav}{2R}$     (B)  $\frac{2Bav}{2R}$     (C)  $\frac{Bav}{2}$     (D)  $\frac{Bav}{4R}$


**Q.26** Finally square frame reduces to straight wire. The total charge flown is

- (A)  $\frac{a^2B}{R}$     (B)  $\frac{a^2B}{2R}$     (C)  $\frac{aB}{R}$     (D)  $\frac{aB}{R}$

**Paragraph 2:** In case of analysis of circuits, containing cells, resistance and inductances two things are very important one is conservation of charge which leads to the fact that at any junction of circuit incoming current is equal to outgoing current. The other thing is that sum of voltage drop in a closed loop is equal to zero. Inductors have a unique property by which they oppose the change in magnetic flux linked to them.

The voltage drop across resistor is  $V_R = IR$  and across inductor is  $L \frac{dI}{dt}$ . In the steady state current through

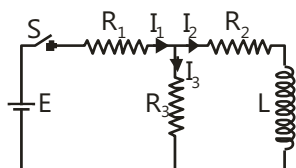inductor becomes constant which leads to zero voltage drop across inductor. i.e. it behaves like short circuit. Refer to circuit (see figure)  $E = 10V$ ,  $R_1 = 2\Omega$ ,  $R_2 = 3\Omega$ ,  $R_3 = 6\Omega$  and  $L = 5H$



**Q.27** The current  $I_1$  just after pressing the switch  $S$  is

- (A)  $\frac{10}{8}A$     (B)  $\frac{10}{5}A$     (C)  $\frac{10}{12}A$     (D)  $\frac{10}{6}A$

**Q.28** The current  $I_1$  long after pressing the switch  $S$  is

- (A)  $\frac{10}{4}A$     (B)  $\frac{10}{5}A$     (C)  $\frac{10}{12}A$     (D)  $\frac{10}{6}A$

**Q.29** The current  $I_2$  long after pressing the switch  $S$  is


- (A)  $\frac{10}{4}A$     (B)  $\frac{10}{5}A$     (C)  $\frac{10}{12}A$     (D)  $\frac{10}{6}A$

**Q.30** The current through  $R_2$  just after releasing the switch  $S$  is

- (A)  $\frac{10}{4}A$     (B)  $\frac{10}{5}A$     (C)  $\frac{10}{6}A$     (D)  $\frac{10}{6}A$

**Match the Columns**

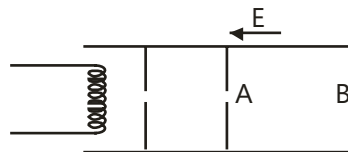
**Q.31** Electrons are emitted by a hot filament and are accelerated by an electric field as shown in figure. The two stops at the left ensure that the electron beam has a uniform cross-section. Match the entries of column-I with column-II as electron move from A to B:



Column-I	Column-II
(A) Speed of an electron	(p) Increase
(B) Number of free Per unit Volume electrons	(q) Decrease
(C) current density	(r) Remains same
(D) Electric potential	(s) any of the above is possible


**Previous Years' Questions**

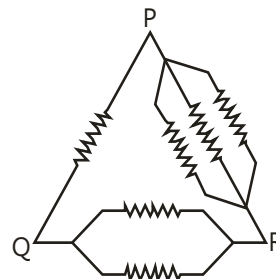**Q.1** Six equal resistance are connected between points P, Q and R as shown in the figure. Then, the net resistance will be maximum between **(2004)**



- (A) P and Q    (B) Q and R  
(C) P and R    (D) Any two points

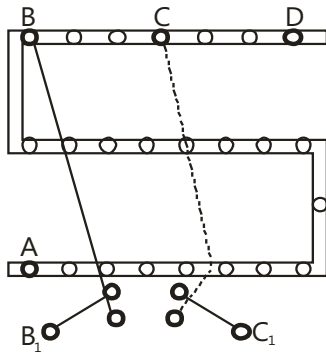**Q.2** For the post office box arrangement to determine the value of unknown resistance, the unknown resistance should be connected between **(2004)**




- (A) B and C
- (B) C and D
- (C) A and D
- (D) B<sub>1</sub> and C<sub>1</sub>

**Q.3** A moving coil galvanometer of resistance  $100\ \Omega$  is used as ammeter using a resistance  $0.1\ \Omega$ . The maximum deflection current in the galvanometer is  $100\ \mu\text{A}$ . Find the current in circuit, so that the ammeter shown maximum deflection **(2005)**


- (A) 100.1 mA
- (B) 1000.1 mA
- (C) 10.01 mA
- (D) 10.1 mA

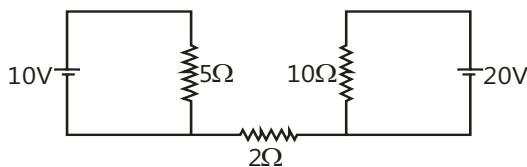**Q.4** Find out the value of current through  $2\ \Omega$  resistance for the given circuit. **(2005)**



- (A) 5A
- (B) 2A
- (C) Zero
- (D) 4A

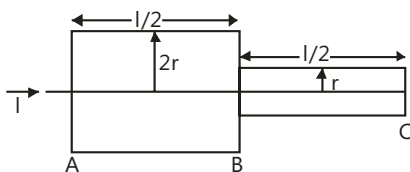
**Q.5** Two bars of radius  $r$  and  $2r$  are kept in contact as shown figure. An electric current  $I$  is passed through the bars. Which one of following is correct? **(2006)**



- (A) Heat produced in bar BC is 4 times the heat produced in bar AB
- (B) Electric field in both halves is equal

- (C) Current density across AB is double that of across BC
- (D) Potential difference across AB is 4 times that of across BC

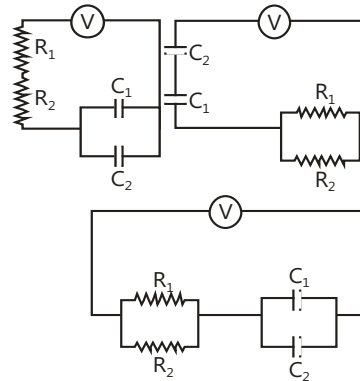
**Q.6** Find the time constant for the given RC circuits in correct (in  $\mu\text{s}$ ). **(2006)**



$R_1 = 1\ \Omega, R_2 = 2\ \Omega, C_1 = 4\ \mu\text{F}, C_2 = 2\ \mu\text{F}.$


- (A) 18, 4, 8/9
- (B) 18, 8/9, 4
- (C) 4, 18, 8/9
- (D) 4, 8/9, 18

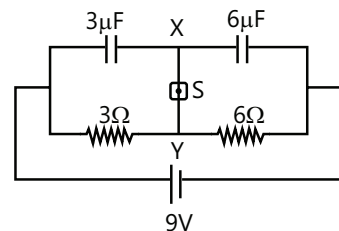**Q.7** A circuit is connected as shown in the figure with the switch S open. When the switch is closed, the total amount of charge that flows from Y to X is **(2007)**




- (A) Zero
- (B)  $54\ \mu\text{C}$
- (C)  $27\ \mu\text{C}$
- (D)  $81\ \mu\text{C}$

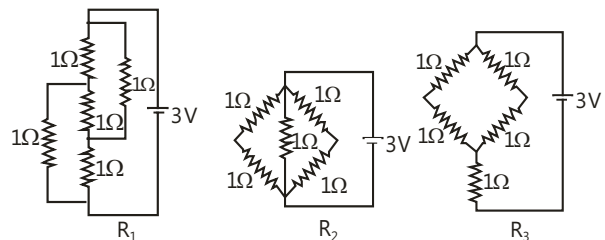**Q.8** Figure shows resistor circuit configuration  $R_1, R_2$  and  $R_3$  connected to 3V battery. If the power dissipated configuration  $R_1, R_2$  and  $R_3$  is  $P_1, P_2$  and  $P_3$  respectively, then **(2008)**



- (A)  $P_1 > P_2 > P_3$
- (B)  $P_1 > P_3 > P_2$
- (C)  $P_2 > P_1 > P_3$
- (D)  $P_3 > P_2 > P_1$

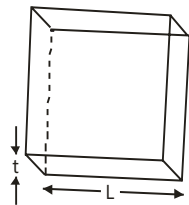**Q.9** Consider thin square sheet of side  $L$  and thickness  $t$ , made of a material of resistivity  $\rho$ . The resistance between two opposite faces, shown by the shaded area in the figure is (2010)



- (A) Directly proportional to  $L$ .
- (B) Directly proportional to  $t$
- (C) Independent of  $L$
- (D) Independent of  $t$

### Assertion Reasoning Type

- (A) If statement-I is true, statement-II is true: statement-II is the correct explanation for statement-I
- (B) If statement-I is true, statement-II is true: statement-II is not a correct explanation for statement-I
- (C) If statement-I is true: statement-II is false
- (D) If statement-I is false: statement-II is true

**Q.10 Statement-I:** In a meter bridge experiment, null point for an unknown resistance is measured. Now, the unknown resistance is put inside an enclosure maintained at a higher temperature. The null point can be obtained at the same point as before by decreasing the value of the standard resistance.

**Statement-II:** Resistance of a metal increases with increase in temperature. (2008)

**Q.11** Capacitor  $C_1$  of capacitance  $1\mu\text{F}$  and capacitor  $C_2$  of capacitance  $2\mu\text{F}$  are separately charged fully by a common battery. The two capacitors are then separately allowed to discharge through equal resistor at time  $t = 0$  (1989)

- (A) The current in each of the two discharging circuits is zero at  $t = 0$
- (B) The current in the two discharging circuits at  $t = 0$  are equal but not zero
- (C) The current in the two discharging circuits at  $t = 0$  are unequal
- (D) Capacitor  $C_1$  loses 50% of its initial charge sooner than  $C_2$  loses 50% of its initial charge


**Q.12** A micrometre has a resistance of  $100\Omega$  and full scale range of  $50\mu\text{A}$ . It can be used as a voltmeter or as a higher range ammeter provided a resistance is added to it. Pick the correct range and resistance combination (S) (1991)

- (A) 50V range with  $10\text{ k}\Omega$  resistance in series
- (B) 10V range with  $200\text{ k}\Omega$  resistance in series
- (C) 5mA range with  $1\Omega$  resistance in parallel
- (D) 10mA range  $1\Omega$  resistance in parallel

**Q.13** When a potential difference is applied across. The current passing through (1999)


- (A) An insulator at 0 K is zero
- (B) A semiconductor at 0 K is zero
- (C) A metal at 0 K finite
- (D) A p-n diode at 300 K is finite, if it is reverse biased

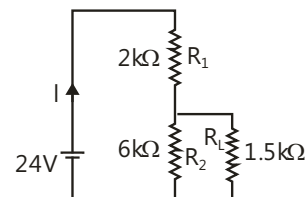**Q.14** For the circuit shown in the figure. (2009)



- (A) The current  $I$  through the battery is 7.5 mA
- (B) The potential difference across  $R_1$  is 18V
- (C) Ratio of powers dissipated in  $R_1$  and  $R_2$  is 3
- (D) If  $R_1$  and  $R_2$  are interchanged, magnitude of the power dissipated in  $R_1$  will decrease by a factor of 9

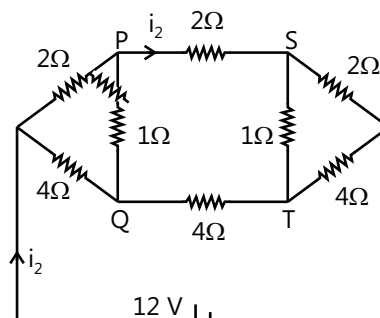**Q.15** For the resistance network shown in the figure, choose the correct option(s). (2012)




- (A) The current through PQ is zero
- (B)  $I_1 = 3\text{ A}$
- (C) The potential at S is less than that at Q
- (D)  $I_2 = 2\text{ A}$




**Q.16** The ideal batteries of emf  $V_1$  and  $V_2$  and three resistances  $R_1$ ,  $R_2$  and  $R_3$  are connected as shown in the figure. The current in resistance  $R_2$  would be zero if  
(2014)

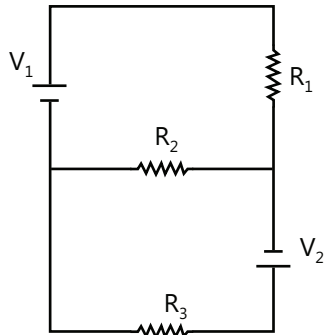- (A)  $V_1 = V_2$  and  $R_1 = R_2 = R_3$   
 (B)  $V_1 = V_2$  and  $R_1 = 2R_2 = R_3$   
 (C)  $V_1 = 2V_2$  and  $2R_1 = 2R_2 = R_3$   
 (D)  $2V_1 = 2V_2$  and  $2R_1 = R_2 = R_3$







**Q.17** During an experiment with a metre bridge, the galvanometer shows a null point when the jockey is pressed at 40.0 cm using a standard resistance of  $90 \Omega$ , as shown in the figure. The least count of the scale used in the metre bridge is 1 mm. The unknown resistance is  
(2014)

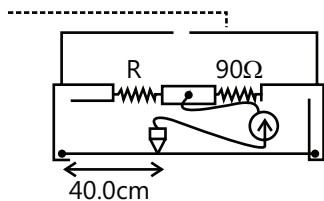- (A)  $60 \pm 0.15 \Omega$       (B)  $135 \pm 0.56 \Omega$   
 (C)  $60 \pm 0.25 \Omega$       (D)  $135 \pm 0.23 \Omega$



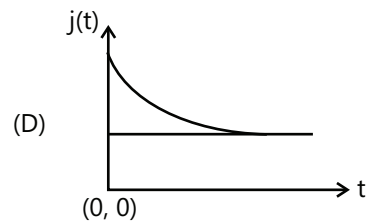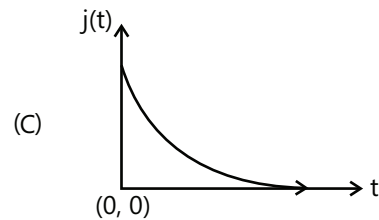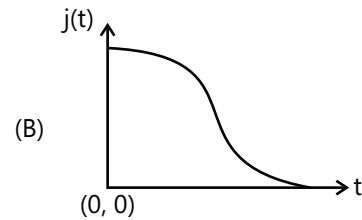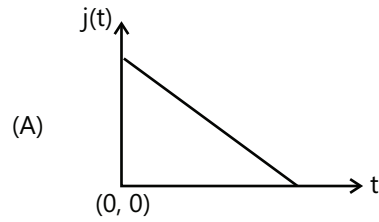
**Q.18** An infinite line charge of uniform electric charge density  $\lambda$  lies along the axis of an electrically conducting infinite cylindrical shell of radius  $R$ . At time  $t = 0$ , the space inside the cylinder is filled with a material of permittivity  $\epsilon$  and electrical conductivity  $\sigma$ . The electrical conduction in the material follows Ohm's law. Which one of the following graphs best describes the subsequent variation of the magnitude of current density  $j(t)$  at any point in the material?  
(2016)



**Q.19** Consider the identical galvanometers and two identical resistors with resistance  $R$ . If the internal resistance of the galvanometers  $R_c < R/2$ , which of the following statement(s) about any one of the galvanometers is(are) true?  
(2016)

- (A) The maximum voltage range is obtained when all the components are connected in series  
 (B) The maximum voltage range is obtained when the two resistors and one galvanometer are connected in series, and the second galvanometer is connected in parallel to the first galvanometer  
 (C) The maximum current range is obtained when all the components are connected in parallel  
 (D) The maximum current range is obtained when the two galvanometers are connected in series and the combination is connected in parallel with both the resistors

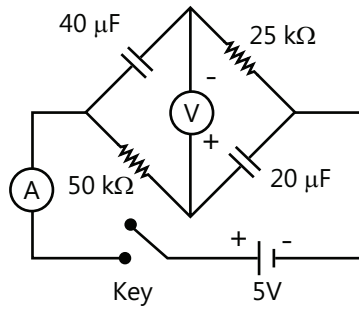**Q.20** In the circuit shown below, the key is pressed at time  $t = 0$ . Which of the following statement(s) is (are) true?  
(2016)



- (A) The voltmeter displays  $-5\text{ V}$  as soon as the key is pressed, and displays  $+5\text{ V}$  after a long time  
 (B) The voltmeter will display  $0\text{ V}$  at time  $t = \ln 2$  seconds  
 (C) The current in the ammeter becomes  $1/e$  of the initial value after 1 second  
 (D) The current in the ammeter becomes zero after a long time

## MASTERJEE Essential Questions

### JEE Main/Boards

#### Exercise 1

Q. 8      Q.9      Q.11  
 Q.19      Q.20      Q.24  
 Q.28

#### Exercise 2

Q. 2      Q.4      Q.8  
 Q.14

### JEE Advanced/Boards

#### Exercise 1

Q.1      Q.2      Q.13  
 Q. 23      Q.24

#### Exercise 2

Q.5      Q.9      Q.14  
 Q.15      Q.17      Q.18  
 Q.21  
 Comprehension – 1 (Q.24-26),  
 Comprehension – 2 (Q.27-30)

## Answer Key

### JEE Main/Boards

#### Exercise 1

**Q.1** 30 A  
**Q.2**  $17\ \Omega$ , 8.5V  
**Q.3** (a)  $6\ \Omega$  (b) 2 V,4V ,6V

**Q.4** (a)  $(20/19)\ \Omega$  ,(b) 10A, 5A, 4A; 19A

**Q.5**  $1027^\circ\text{C}$

**Q.6**  $2.0 \times 10^{-7}\ \Omega\text{ m}$

**Q.7**  $0.0039^\circ\text{C}^{-1}$

**Q.8**  $867^\circ\text{C}$

**Q.9** current in branch AB =  $(4/17)A$ , in BC =  $(6/17)A$ , in CD =  $(-4/17)A$ , in AD  $(6/17)A$ , in BD =  $(-2/17)A$ , total current  $(10/17)A$ .

**Q.10** 11.5V

**Q.11** 2.25V

**Q.12**  $2.7 \times 10^4$  s (7.5 h)

**Q.13**  $\approx 238$  s.

**Q.14** (a) 1.4A, 11.9V, (b) 0.005 A

**Q.15**  $\approx 22$  Aluminium is lighter, it is preferred for long suspensions of cables

**Q.16** (a) Only current (because it is given to be steady). The rest depends on the area of cross-section inversely.

(b) No, examples of non-ohmic elements; vacuum diode, semiconductor diode.

(c) Because the maximum current drawn a source =  $\varepsilon/r$ .

(d) Because, if the circuit is shorted (accidentally), the current drawn will exceed safety limits, if internal resistance is not large

**Q.17** (a) greater, (b) lower, (c) nearly independent of, (d)  $10^{22}$ .

**Q.18** Hint: Let X be the equivalent resistance of the infinite network. Clearly,  $2+X(X+1) = X$  which given  $X = (1 + \sqrt{3}) \Omega$ ; therefore the current is 3.7 A

**Q.19** (a)  $\varepsilon = 1.24V$ , (b) To reduce current through the galvanometer when the movable contact is far from the balance point, (c) No. (d) N truncated. (e) No

**Q.20**  $1.7 \Omega$

**Q.21** Resistance in series =  $5988 \Omega$

**Q.22** Shunt resistance =  $10 \text{ m}\Omega$

**Q.23** 0.12 volt

**Q.24** (a) 0.9 A, (b)(b) Yes we can do it. It is called Thevenin theorem. It can be represented as equivalent resistance and equivalent voltage.

**Q.25** (a) shunt resistance =  $400 \times 10^{-3}$  which is also nearly its net resistance, reads slightly less. (b) Series resistance =  $3988 \Omega$ ; net resistance =  $4000 \Omega$ ; read slightly less

**Q.26**  $2 \Omega, 4 \Omega$

**Q.27** 3.6 volt

## Exercise 2

### Single Correct Choice Type

**Q.1** D

**Q.2** C

**Q.3** B

**Q.4** B

**Q.5** D

**Q.6** C

**Q.7** C

**Q.8** D

**Q.9** C

**Q.10** A

**Q.11** D

**Q.12** C

**Q.13** D

**Q.14** B

**Q.15** C

**Q.16** D

**Q.17** D

**Q.18** C

### Previous Years' Questions

**Q.1** B

**Q.2** C

**Q.3** B

**Q.4** D

**Q.5** A

**Q.6** C

**Q.7** B

**Q.8** C

**Q.9** A

**Q.10** A

**Q.11** A

**Q.12** D

**Q.13** C

**Q.14** C

**Q.15** C

**Q.16** A

**Q.17** B

**Q.18** C

**Q.19** D

## JEE Advanced/Boards

### Exercise 1

**Q.1**  $1 \Omega$

**Q.2**  $I = 2.5A, V = 2.5 V$

**Q.3**  $\frac{22}{35} \Omega$

**Q.4** 12A-20W

**Q.5**  $\sqrt{R_1 R_2}$

**Q.6**  $\frac{3r}{5} \Omega$

Q.7  $4\ \Omega$

Q.10  $20/3\text{V}$

Q.13  $46.67\ \text{cm}$

Q.16  $20\ \text{ohm}$

Q.19  $\frac{R_1}{R_2} = \frac{5}{3}$

Q.21 (i)  $\frac{(k-1)^2}{k}; \frac{k}{(k-1)}$  (ii)  $\frac{((k-1) \setminus k^2)V_0}{R^3}$

Q.23 (i)  $V_{ab} = -12\ \text{V}$  (ii) 3 amp from b to a

Q.24  $R = \frac{\rho_0 L}{A} \left(1 - \frac{1}{e}\right); I = \frac{V_0 A}{\rho_0 L} \left(\frac{e}{e-1}\right); V = \frac{V_0(e^{-x/L} - e^{-1})}{1 - e^{-1}}$  Q.25  $7.2\ \text{m}$

Q.8  $1\ \Omega$

Q.11  $7.5\ \text{A}$

Q.14  $4\ \text{ohm}$

Q.17  $7.5\ \text{m}, 8.7\ \text{m}, 6.125\ \text{m}$

Q.20 (i)  $10.52\ \Omega$ ; (ii)  $0.3125\ \Omega$

Q.9  $600\ \Omega$

Q.12  $1\text{V}$

Q.15  $\frac{10}{3}\ \Omega, 5\ \Omega$

Q.18 (a)  $J_0 A \sqrt{3}$ ; (b)  $2J_0 A \sqrt{3}$

Q.22  $4/9\ \text{kgs}^{-1}, 450\ \text{sec}$

## Exercise 2

### Single Correct Choice Type

Q.1 D

Q.2 B

Q.3 B

Q.4 A

Q.5 B

Q.6 B

Q.7 A

Q.8 C

Q.9 C

Q.10 C

Q.11 B

Q.12 D

Q.13 A

Q.14 C

### Multiple Correct Choice Type

Q.15 A, B, C, D

Q.16 A, D

Q.17 B, C

Q.18 A, B, C

Q.19 A, D

Q.20 A, D

### Assertion Reasoning type

Q.21 D

Q.22 D

Q.23 A

### Comprehension Type

Q.24 B

Q.25 B

Q.26 A

Q.27 A

Q.28 A

Q.29 D

Q.30 C

### Match the Columns

Q.31 A  $\rightarrow$  p, B  $\rightarrow$  q, C  $\rightarrow$  r, D  $\rightarrow$  p

## Previous Years' Questions

Q.1 A

Q.2 C

Q.3 A

Q.4 C

Q.5 A

Q.6 B

Q.7 C

Q.8 C

Q.9 C

Q.10 D

Q.11 B, D

Q.12 B, C

Q.13 A, B, D

Q.14 A, D

Q.15 A, B, C, D

Q.16 A, B, D

Q.17 C

Q.18 C

Q.19 A, C

Q.20 A, B, C, D

## Solutions

### JEE Main/Boards

#### Exercise 1

**Sol 1:**  $i = \frac{V}{R} = \frac{12}{0.4} = 30 \text{ A}$

**Sol 2:**  $i = \frac{V}{r+R}$  (let R be resistor)

$$0.5 = \frac{10}{3+R}$$

$$R = 17 \Omega$$

$$V_0 = V - ir = 10 - 3(0.5) = 8.5 \text{ V}$$

$$\therefore \text{Terminal voltage} = 8.5 \text{ V}$$

**Sol 3:** (a)  $r = r_1 + r_2 + r_3 = 1 + 2 + 3 = 6 \Omega$

(B)  $i = \frac{V}{r} = \frac{12}{6} = 2 \text{ A}$

$$V = ir = i[1, 2, 3] = 2[1, 2, 3] = [2, 4, 6]$$

$$\therefore \text{Potential drops are } 2\text{V}, 4\text{V}, 6\text{V}$$

**Sol 4:**  $\frac{1}{R} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$

$$\frac{1}{R} = \frac{19}{20}$$

$$\Rightarrow R = \frac{20}{19} \Omega$$

$$i = V \left( \frac{1}{r} \right) = 20 \left[ \frac{1}{2} \frac{1}{4} \frac{1}{5} \right] = [10 \ 5 \ 4]$$

$$\therefore \text{Current is } 10\text{A}, 5\text{A}, 4\text{A}$$

$$\text{Total current} = \frac{V}{R} = \frac{20}{\frac{20}{19}} = 19 \text{ A}$$

**Sol 5:**  $r_t = r_0 + \alpha(t - t_0)$

$$117 = 100 + 1.7 \times 10^{-4} \Delta t$$

$$\Rightarrow \Delta t = 10^3 \text{ }^\circ\text{C}$$

$$\Rightarrow t_0 = t_0 + \Delta t = 27 + 10^3$$

$$t = 1027^\circ\text{C}$$

**Sol 6:**  $R = \frac{\rho L}{A}$

$$\rho = \frac{RA}{L} = \frac{5 \times 6 \times 10^{-7}}{15} = 2 \times 10^{-7} \Omega\text{m}$$

**Sol 7:**  $\alpha = \frac{\Delta r}{\Delta t} = \frac{2.7 - 2.1}{100 - 27.5} = 0.0039^\circ\text{C}^{-1}$

**Sol 8:**  $\alpha = \frac{\Delta r}{\Delta t} = \frac{\frac{V}{i_1} - \frac{V}{i_2}}{\Delta t} = \frac{V}{\Delta t} \left( \frac{1}{i_1} - \frac{1}{i_2} \right)$

$$t = t_0 + \frac{V}{\alpha} \left( \frac{1}{i_1} - \frac{1}{i_2} \right) = 27 + \frac{230}{1.7 \times 10^{-4}} \left( \frac{1}{2.8} - \frac{1}{3.2} \right)$$

$$= 867^\circ\text{C}$$

**Sol 9:** By symmetry  $i_{AB} = i_{DC}$

$$i_{BC} = i_{AD}$$

Let current in circuit be  $i$

$$\text{Let } i_{AB} = i_1$$

$$(i - i_1)_5 = 10(i_1) + 5(i_1 - (i - i_1))$$

(from ABD)

$$Si - Si_1 = 10i_1 + 10i_1 - 5i$$

$$\Rightarrow 25i_1 = 10i$$

$$\Rightarrow i_1 = \frac{2}{5}i$$

$$\text{Now, } 10 = 10i + 10i_1 + 5(i - i_1)$$

$$= 15i + 5i_1 = 15i + \frac{2}{5}i_1(5)$$

$$10 = 17i$$

$$i = \frac{10}{17} \text{ A}$$

$$i_{AB} = i_{OC} = \frac{2}{3}i = \frac{4}{17} \text{ A}$$

$$i_{AD} = i_{BC} = i - i_1 = \frac{6}{17} \text{ A}$$

$$i_{CD} = 2i_1 - i = \frac{-4}{17} \text{ A}$$

$$\text{Sol 10: } i = \frac{V_1 - V_2}{R + r} = \frac{120 - 8}{15.5 + 0.5}$$

$$i = 7 \text{ A}$$

$$\Delta V_{\text{battery}} = V + ir = 8 + 7(0.5) = 11.5 \text{ V}$$

$$\text{Sol 11: } \frac{V_1}{V_2} = \frac{\ell_1}{\ell_2}$$

$$\Rightarrow V_2 = V_1 \times \frac{\ell_2}{\ell_1} = 1.25 \times \frac{63}{35} = 2.25 \text{ V}$$

$$\text{So 12: } \frac{I}{A} = neV_d; \quad V_d = \frac{I}{Ane}$$

$$t = \frac{\ell}{V_d} = \frac{Ane\ell}{I} = \frac{2 \times 10^{-6} \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 3}{3}$$

$$= 27200 \text{ sec}$$

$$\text{Sol 13: } Q = \sigma A = \sigma \cdot \frac{4}{3} \pi r_e^3$$

$$t = \frac{Q}{i} = \frac{4 \pi \sigma r_e^3}{3 i} = \frac{4 \pi \times 10^{-9} \times (6.37 \times 10^6)^3}{1800}$$

$$\approx 238 \text{ s}$$

$$\text{Sol 14: (a) } i = \frac{nV}{R + nr} = \frac{6 \times 2}{8.5 + 6(0.015)} = 1.4 \text{ A}$$

$$\text{Terminal voltage} = iR = 1.4(8.5) = 11.9 \text{ V}$$

$$(b) i_{\text{max}} = \frac{V}{r} = \frac{1.9}{380} = 0.005 \text{ A}$$

It can't start a car as its current is very less.

$$\text{Sol 15: } R = \frac{\rho \ell}{A}; \quad R \propto \frac{\rho}{A}$$

$$m = dAl$$

$$A \propto \frac{m}{d}; \quad \frac{1}{A} \propto \frac{d}{m}$$

$$\Rightarrow R \propto \frac{\rho d}{m} \quad R = \text{constant}$$

$$\Rightarrow m \propto \rho d$$

$$\frac{m_{\text{Al}}}{m_{\text{Cu}}} = \frac{2.63 \times 10^{-8} \times 2.7}{1.72 \times 10^{-8} \times 8.9} = 0.464$$

$$\Rightarrow m_{\text{Al}} < m_{\text{Cu}}$$

Aluminium is lighter

For long suspension cables, Al is used as it is lighter.

**Sol 16:** (a) Only current is constant. Rest depends on area of cross-section inversely.

(b) Ohm's law is non-universal for example non-ohmic conductors like semi-conductors.

$$(c) i = \frac{E}{r} \Rightarrow i \propto \frac{1}{r}$$

So low resistance is necessary.

(d) Because the circuit is shorted accidentally, the current drawn will exceed safely limits.

**Sol 17:** (a) Alloys have greater resistance than their constitutional metals.

(b) Alloys have lower temperature coefficient of resistance than pure metals.

(c) It is nearly independent


$$(d) r = \frac{\rho \ell}{A} \Rightarrow \frac{r_1}{r_2} = \frac{\rho_1}{\rho_2}$$

$$r \gg \gg r_2 \Rightarrow \rho_1 \gg \gg \rho_2$$

$\Rightarrow 10^{22}$  is the correct answer.

Note: (a), (b), (c) are all theoretical. Perfect reasoning will be learnt in engineering. You may refer to energy bands to understand it.

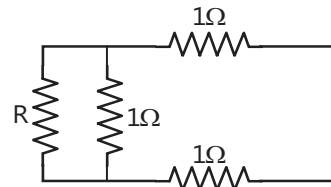**Sol 18:** Let the resistance of circuit be R.



$$\Rightarrow R = \frac{1}{\frac{1}{R} + \frac{1}{1}} + 2 \Rightarrow R = \frac{R}{R+1} + 2$$

$$\Rightarrow R = \sqrt{3} + 1; \quad (R > 0 \Rightarrow R \neq -\sqrt{3} + 1)$$

$$i = \frac{V}{r+R} = \frac{12}{\sqrt{3} + 1 + 0.5} \approx 3.7 \text{ A}$$

**Sol 19:** (a) Let length of potentiometer be  $\ell$

$\Rightarrow$  Standard cell voltage

$$V_s = \frac{\ell_2}{\ell} E$$

Assume  $\ell = 100 \text{ cm}$

For standard potentiometer

$$\Rightarrow \xi = \frac{1.02 \times 100}{82.3} = 1.24 \text{ V}$$

(b) 600 k $\Omega$  is used to reduce the galvanometer current, when the movable contact is far from the balance point.

(c) No, the balance point where voltage of standard cell equals voltage difference of potentiometer. Hence current is zero so high resistance doesn't affect it.

(d) Not much if the driver cell has small resistance compared to potentiometer. Else it affects

(e) No, as emf of driver cell is less than standard cell, current through galvanometer is in opposite direction.

(f) No, if doesn't work well as the gradation on potentiometer is low. To measure it keep a high resistance in series to battery, to reduce voltage across potentiometer.

**Sol 20:** For  $\ell_1 = 76.3 \text{ cm}$ ,  $V_1 = 1.5 \text{ V}$

$$\Rightarrow V_2 = \frac{\ell_2}{\ell_1} \times V_1 = \frac{64.8}{76.3} \times 1.5 = 1.274 \text{ V}$$

Let current in 9.5 $\Omega$  be  $i$

$$\Rightarrow (9.5) (i) = 1.27 \text{ V} \Rightarrow i = 0.134 \text{ A}$$

$$\Rightarrow 1.274 = 1.5 - i(r)$$

$$\Rightarrow r = 1.7 \text{ } \Omega$$

**Sol 21:** Voltage across galvanometer

$$(V) = ir = 3 \times 10^{-3} \times 12 = 36 \text{ mV}$$

To convert it into a voltmeter of maximum value  $V_0$ , resistance  $R$  should be added in series.

$$V_0 = 18 \text{ V}$$

$$\therefore V_0 \gg V \Rightarrow R \gg r$$

$$\Rightarrow R = \frac{V_0}{i} = \frac{1.8}{3 \times 10^{-3}} \approx 6 \text{ k}\Omega$$

For accurate result, use

$$V_0 = i(r + R) \Rightarrow R = 5988 \text{ } \Omega$$

**Sol 22:**  $i_1 R_1 = i_2 R_2$

$$\Rightarrow R_2 = \frac{i_1 R_1}{i_2} = \frac{4 \times 10^{-3} \times 15}{6} = 10^{-2} \Omega = 10 \text{ m}\Omega$$

**Sol 23:** Potential gradient =  $\frac{\Delta V_p}{\ell}$

( $\Delta V_p$  = Potential across potentiometer)

$$\Delta V_p = \frac{r_p \times \varepsilon}{r_p + R} = \frac{20 \times 5}{20 + 480} = 0.2 \text{ V}$$

$$\text{Potential gradient} = \frac{0.2}{10} = 2 \times 10^{-2} \text{ V/m}$$

$$E = \text{Potential gradient} \times \text{length}$$

$$= 2 \times 10^{-2} \times 6 = 0.12 \text{ V}$$

$$\text{Sol 24: (a) } i = \frac{V_1 + V_2 + V_3}{r_1 + r_2 + r_3 + R}$$

$$= \frac{2 + 1.8 + 1.5}{0.05 + 0.71 + 1 + 4} = 0.9 \text{ A}$$

(b) Yes we can do it. It is called theorem. It can be represented as equivalent resistance and equivalent voltage.

**Sol 25:** (a) The resistance to be added in parallel

$$r_s = \frac{r \cdot i}{i_A} = \frac{12 \times 2.5 \times 10^{-3}}{7.5} = 4 \times 10^{-3} \Omega = 4 \text{ m}\Omega$$

$\therefore$  Shunt resistance is 4 m $\Omega$

(b) The resistance to be added in series

$$R = \frac{V}{i} = \frac{10}{2.5 \times 10^{-3}} = 4 \text{ k}\Omega$$

$$\therefore r_{\text{series}} = r - r_g = 4000 - 12 = 3988 \text{ } \Omega$$

Ammeter reads slightly less as all of  $i_A$  doesn't pass through shunt. In derivation we assume  $i_A$  passes through shunt only for full deflection. Hence it reads slightly less. Voltmeter reads less as some current passes through it, which reduces current in the measuring element, which leads to reduced reading.

$$\text{Sol 26: } \frac{R_1}{R_2} = \frac{\frac{1}{3}}{1 - \frac{1}{3}} = \frac{1}{2} \Rightarrow R_2 = 2R_1$$

$$\frac{R_1 + 6}{R_2} = \frac{\frac{2}{3}}{1 - \frac{2}{3}} = 2$$

$$\Rightarrow \frac{R_1 + 6}{2R_1} = 2 \Rightarrow R_1 = 2 \Omega, R_2 = 4 \Omega,$$

**Sol 27:** Let current in each branch be  $i$

Current in 10 $\Omega$  is  $2i$  by symmetry

$$\Rightarrow 2 + 2 = 10(2i) + 2 \times 1.05 (i)$$

$$i = \frac{4}{22.1} = 0.181 \text{ A}$$

$$V_{10\Omega} = 20i = 3.6 \text{ V}$$

**Sol 28:** Let  $V_D = 0$

$$3V - 1V = i_1(3 + 1) + 2I \text{ (for loop BDC)}$$

$$1V - 2V = i_2(2 + 1) + 2I \text{ (for loop BDA)}$$

$$I = i_1 + i_2$$

$$\Rightarrow 2V = i_1(4) + 2(i_1 + i_2)$$

$$\Rightarrow 6i_1 + 2i_2 = 2$$

$$\Rightarrow -1V = 3i_1 + 2(i_1 + i_2)$$

$$\Rightarrow 2i_1 + 5i_2 = -1$$

$$\Rightarrow i_2 = \frac{-5}{13} \text{ A (from (i) and (ii)) } i_1 = \frac{6}{13}$$

$$V_D - V_B = -2(I) = -2(i_1 + i_2)$$

$$= -2\left(\frac{6}{13} - \frac{5}{13}\right) = \frac{-2}{13} \text{ V}$$

$$\Delta V_G = E_G - i_1 R_G = 3V - \frac{6}{13} \text{ (iii)} = \frac{21}{13} \text{ V}$$

$$\Delta V_H = E_H + i_1 R_H = 1 + \frac{16}{13} \text{ (i)} = \frac{19}{13} \text{ V}$$

## Exercise 2

### Single Correct Choice Type

**Sol 1 : (D)**  $i = neVA$

$$\frac{i_1}{i_2} = \frac{V_1 A_1}{V_2 A_2}$$

$$i_1 = i_2$$

$$\Rightarrow V_1 A_1 = V_2 A_2$$

$$V_1(\pi d^2) = V_2\left(\frac{\pi d^2}{4}\right); V_2 = 4V$$

**Sol 2 : (C)**  $i = neVA$

$\therefore$  For constant  $n$  and  $e$ ;

$$\Rightarrow V_1 A_1 = V_2 A_2$$

$$\frac{V_p}{V_Q} = \frac{A_Q}{A_p}; A_Q > A_p$$


$$\therefore \frac{V_p}{V_Q} > 1; \Rightarrow V_p > V_Q$$

**Sol 3 : (B)**  $i = neVA$

$$V = \frac{i}{neA} = \frac{i}{pqS}$$

**Sol 4 : (B)**  $V = iR$

$$\frac{V}{i} = R$$

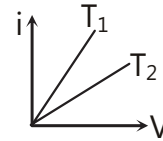

... (i)

... (ii)


Here slope of the graph is  $\left(\frac{i}{V}\right) = \left(\frac{1}{R}\right)$

We know that as temperature increases, Resistance of the metal increases.

$$\therefore \left(\frac{1}{R_1}\right) > \left(\frac{1}{R_2}\right) \text{ [From graph]}$$

$$\Rightarrow R_1 < R_2 \therefore T_1 < T_2$$

**Sol 5 : (D)**

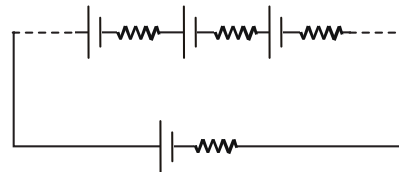


$$i = \left(\frac{E_1 + E_2 + \dots + E_n}{r_1 + r_2 + r_3 + \dots + R}\right)$$

$$i = \frac{nE}{nr} \text{ (for no } R)$$

$$i = \frac{E}{r}$$

**Sol 6 : (C)** On simplifying

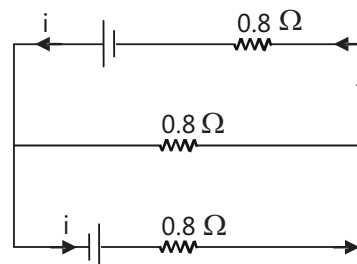

Current flowing through  $R$  is zero.

$$'i' \text{ in the circuit is } \frac{8}{1.6} = 5 \text{ amp.}$$




Potential difference between each cell is  $E - ir$

$$1 - 5(0.2) = 0V$$

**Sol 7 : (C)**  $i = \left( \frac{3+15}{1+2+R} \right)$

$$i = \left( \frac{18}{3+R} \right)$$

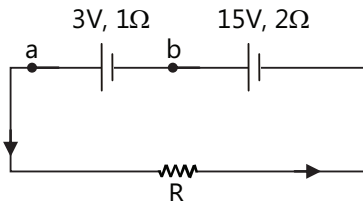


Now writing the potential drop ab;

$$3 - (1) \left( \frac{18}{3+R} \right) = 0$$

$$\Rightarrow 3 = \frac{18}{3+R}; R = 3 \Omega$$

**Sol 8 : (D)**

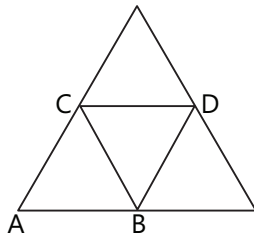

$$R_{CD} = \frac{1}{\frac{1}{2R} + \frac{1}{R}} = \frac{2R}{3}$$

Similarly  $R_{DB} = \frac{4^2 R}{3}$

$$R_{CB} = \frac{1}{\frac{1}{R} + \frac{1}{\frac{2R}{3} + \frac{2R}{3}}}; R_{CB} = \frac{4R}{7}$$

$$R_{AB} = \frac{1}{\frac{1}{R} + \frac{1}{\frac{4R}{7} + R}}; R_{AB} = \frac{11R}{18}$$

**Sol 9 : (C)**  $R = \frac{V^2}{P} \Rightarrow R \propto V^2$

$\therefore$  Connected in series, they have same current  $i$

Power consume ( $P_c$ ) =  $i^2 R$

$$P_c \propto R \Rightarrow P_c \propto V^2$$

**Sol 10 : (A)** (i)  $i_1 = \frac{P_1}{V_1} = \frac{25}{220} \approx 0.1136 \text{ A}$

$$i_2 = \frac{P_2}{V_2} = \frac{100}{220V} \approx 0.4545 \text{ A}$$

$$r_1 = \frac{V_1^2}{P_1} = \frac{200^2}{25} = 1936 \Omega$$

$$r_2 = \frac{V_2^2}{P_2} = \frac{200^2}{100} = 484 \Omega$$

$$i = \frac{V}{r_1 + r_2} = \frac{440}{1936 + 484} = 182 \text{ A}$$

$\therefore$  25 W bulb fuses.

(ii) Alternative solution

$$r \propto \frac{1}{P}$$

$$r_1 : r_2 = P_2 : P_1 = 700 : 25 = 4 : 1$$

$$V_1 : V_2 = r_1 : r_2 = 4 : 1$$

$$V_1 = \frac{4V}{4+1} = \frac{4}{5}V = 352 \text{ V}$$

$$V_2 = \frac{V}{4+1} = \frac{V}{5} = 88 \text{ V}$$

$$V_1 > V_{\text{rated}}, V_2 < V_{\text{rated}}$$

Hence 25W bulb fuses.

**Sol 11: (D)**  $V = \frac{RV}{r+R}$

**Sol 12 : (C)** Let resistance be  $r$

$$i = \frac{V_G - V}{r+R}$$

$$10 = \frac{120 - 100}{r+1}$$

$$\Rightarrow r = 1 \Omega$$

**Sol 13: (D)** Let voltage across galvanometer be  $V$ , resistance  $r$

$$i_1 = \frac{V}{r}$$

Now after shunning

$$i_2 = \frac{V}{r+20}$$

$$\text{given } i_2 = \frac{i_1}{2}$$

$$\Rightarrow \frac{1}{2} \left( \frac{1}{r} \right) = \frac{1}{r+20}$$

$$\Rightarrow r = 20 \Omega$$

**Sol 14: (B)** To convert galvanometer to ammeter, we need to connect resistance across it. Let it be  $r$  max current through galvanometer

$$I = \frac{V}{R} = \frac{0.2}{20} = 10^{-2} \text{ A}$$

$$ir = I_0 R_0$$

$$10(r) = 10^{-2} \times 20$$

$$\Rightarrow r = 2 \times 10^{-2} \Omega$$

$\therefore 0.02 \Omega$  resistor is connected across it.

**Sol 15: (C)** Total voltage ( $V_0$ ) =  $i(r + R)$

$$= 10(90 + 910) \text{ mV} = 10 \text{ V}$$

$\therefore$  Number of divisions

$$= \frac{V_0}{\text{least count}} = \frac{10}{0.1} = 100$$

**Sol 16: (D)**  $V = i(r + R)$

$$12 = 0.1(20 + r) \Rightarrow r = 100 \Omega$$

**Sol 17: (D)** Resistance of galvanometer,

$$R_g \gg r, R$$


$$\therefore V_g \approx 12 \text{ V}$$

$\therefore$  It reads 12 V

**Sol 18: (C)** On increase in temperature, number of free electrons increase. But also the collisions will increase. Hence conductivity decreases.
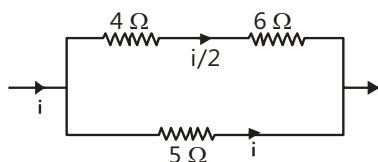
## Previous Years' Questions

**Sol 1: (B)** Sing, resistance in upper branch of the circuit is twice the resistance in low lower branch. Hence, current there will be half.




$$\text{Now } P_4 = (i/2)(4)(p = i^2 R)$$

$$P_5 = (i)^2(5)$$


$$\text{or } \frac{P_4}{P_5} = \frac{1}{5} \quad P_4 = \frac{P_5}{5} = \frac{10}{5} = 2 \text{ cal/s}$$

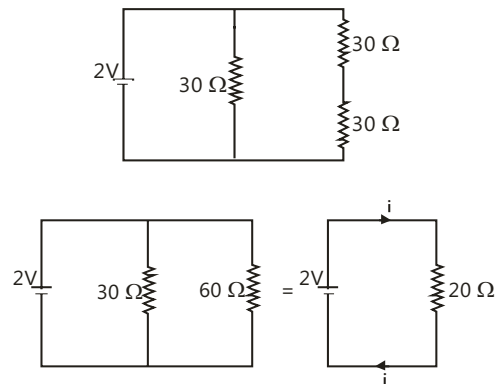**Sol 2: (C)** The simplified circuit is shown in the figure




$$\text{Therefore current } I = I = \frac{2}{20} = \frac{1}{10} \text{ A}$$

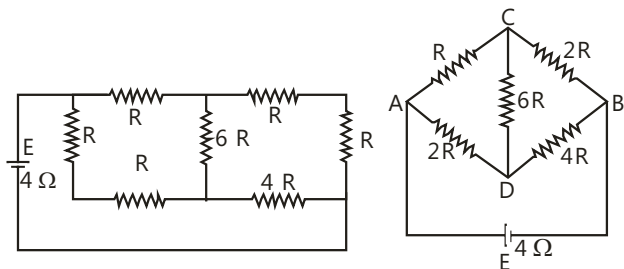**Sol 3: (B)** The given circuit is a balanced Whetstone's bridge



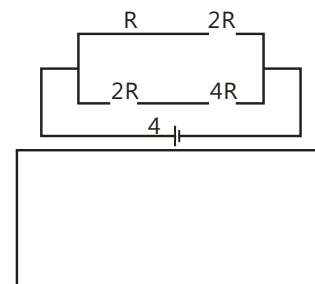Thus no current will flow across  $6R$  of the side  $CD$ . The given circuit will now be equivalent to



For maximum power net external resistance

$$= \text{Total internal resistance}$$


$$\text{or } 2R = 4 \text{ or } R = 2 \Omega$$

**Sol 4: (D)** Net resistance of the circuit is  $9 \Omega$ .

$\therefore$  Current drawn from the battery.

$$= \frac{9}{9} = 1\text{A} = \text{current through } 3 \Omega \text{ resistor}$$
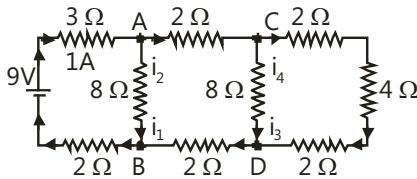
$$\frac{P_{R_1}}{P_{R_2}} = \frac{(I_{R_1}^2)R_1}{(I_{R_2}^2)R_2} = \frac{(7.5)^2(2)}{(1.5)^2(3)} = \frac{25}{3}$$



Potential difference between A and B is

$$V_A - V_B = 9 - (3 + 2) = 4\text{V} - 8i_1$$

$$\therefore i_1 = 0.5 \text{ A}$$

$$\therefore i_2 = 1 - i_1 = 0.5 \text{ A}$$

Similarly potential difference between C and D

$$V_C - V_D = (V_A - V_B) - i_2(2 + 2)$$

$$= 4 - 4i_2 = 4 - 4(0.5) = 2\text{V} = 8i_3$$

$$i_3 = 0.25 \text{ A}$$

$$i_4 = i_2 - i_3 = 0.5 - 0.25$$

$$i_4 = 0.25 \text{ A}$$

**Sol 5: (A)** As there is no change in the reading of galvanometer with switch S open or closed. It implies that bridge is balanced. Current through S is zero and

$$I_R = I_G, I_P = I_Q$$

**Sol 6: (C)** The statement indicates a balanced Wheatstone bridge formed by  $R_3, R_4, R_2$  and  $R_1$ .

$$\Rightarrow \frac{R_3}{R_4} = \frac{R_1}{R_2}$$

i.e.  $R_1 R_4 = R_3 R_2$

**Sol 7: (B)** In the first case  $\frac{(3E)^2}{R} t = ms \Delta T$  ... (i)

$$\left[ H = \frac{V^2}{R} t \right]$$

When length of the wire is doubled, resistance and mass both are doubled.

Therefore, in the second case,

$$\frac{(NE)^2}{2R} t = (2m)s \Delta T \quad \dots (ii)$$

Dividing Eq. (ii) by (i), we get

$$\frac{N^2}{18} = 2 \text{ or } N^2 = 36 \text{ or } N = 6$$


**Sol 8 (C)** In steady state condition, no current will flow through the capacitor C, current in the outer circuit,

$$i = \frac{2V - V}{2R + R} = \frac{V}{3R}$$

Potential difference between A and B


$$V_A - V + V + ir = V_B$$
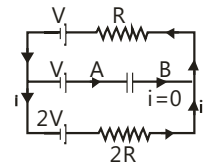
$$\therefore V_B - V_A = iR = \left( \frac{V}{3R} \right) R = \frac{V}{3}$$



**Note:** In this problem charge stored in the capacitor can also be asked. Which is equal to  $q = C \frac{V}{3}$  with positive charge on B side and negative on A side because  $V_B > V_A$

**Sol 9: (A)** The circuit can be drawn as follows:

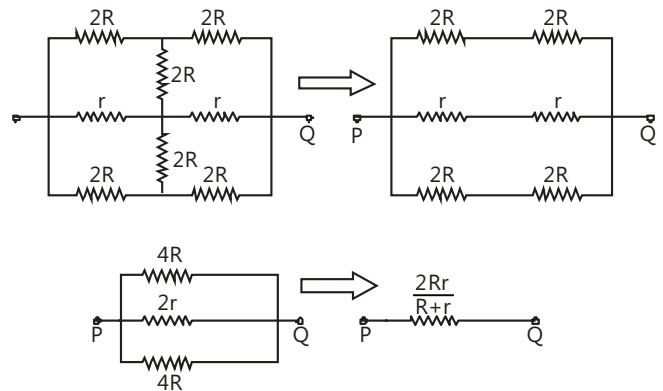

**Sol 10: (A)** The ratio  $\frac{AC}{CB}$  will remain unchanged.

**Sol 11: (A)**  $P = i^2 R$

Current is same, so  $P \propto R$ .

In the first case it is  $3r$ , in second case it is  $\frac{2}{3}r$  in third case it is  $\frac{r}{3}$  and in fourth case the net resistance is  $\frac{3r}{2}$ .

$$R_{III} < R_{II} < R_{IV} < R_I \therefore P_{III} < P_{II} < P_{IV} < P_I$$

**Sol 12: (D)** For discharging of an RC circuit,

$$V = V_0 e^{-t/\tau}$$

$$\text{So, when } V = \frac{V_0}{2}$$

$$\frac{V_0}{2} = V_0 e^{-t/\tau}$$

$$\ln \frac{1}{2} = -\frac{t}{\tau} \Rightarrow \tau = \frac{t}{\ln 2}$$

From graph when  $V = \frac{V_0}{2}$ ,  $t = 100$  s

$$\therefore \tau = \frac{100}{\ln 2} = 144.3 \text{ sec}$$

**Sol 13: (C)** Resistances of both the bulbs are

$$R_1 = \frac{V^2}{P_1} = \frac{220^2}{25}$$

$$R_2 = \frac{V^2}{P_2} = \frac{220^2}{100}$$

Hence  $R_1 > R_2$

When connected in series, the voltages divide in them in the ratio of their resistances. The voltage of 440 V divides in such a way that voltage across 25 W bulb will be more than 220 V.

**Sol 14: (C)** Resistance of bulb =  $\frac{120 \times 120}{60} = 240 \Omega$

Resistance of Heater =  $\frac{120 \times 120}{240} = 60 \Omega$

Voltage across bulb before is switched on,

$$V_1 = \frac{120}{246} \times 240$$

Voltage across bulb after heater is switched on,

$$V_2 = \frac{120}{54} \times 48$$

Decrease in the voltage is  $V_1 - V_2 = 10.04$  V (approximately).

Note: Here supply voltage is taken as rated voltage.

**Sol 15: (C)** For ammeter,  $S = \frac{I_g G}{I - I_g}$

So for I to increase, S should decrease, so additional S can be connected across it.

**Sol 16: (A)**

Item	No.	Power
40 W bulb	15	600 Watt
100 W bulb	5	500 Watt
80 W fan	5	400 watt
1000 W heater	1	1000 Watt

Total Wattage = 2500 Watt

So current capacity


$$i = \frac{P}{V} = \frac{2500}{220} = \frac{125}{11} = 11.36 \approx 12 \text{ Amp}$$

**Sol 17: (B)** Taking the potential at Q to be 0 and at P to be V, we apply Kirchhoff's current law at Q :

$$\frac{V+6}{3} + \frac{V}{1} + \frac{V-9}{5} = 0$$

$$V = -\frac{3}{23} = -0.13 \text{ volt}$$

The current will flow from Q to P.

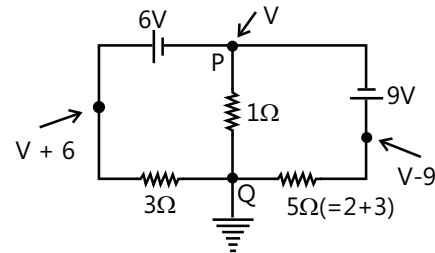

**Sol 18: (C)**  $J = ne v_d$

$$\frac{A \Delta V}{\rho l A} = nev_d$$

$$\therefore \rho = \frac{\Delta v}{lnev_d}$$

$$= \frac{5}{0.1 \times 8 \times 10^{28} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-4}} = 1.56 \times 10^{-4}$$

$$\approx 1.6 \times 10^{-5} \Omega \text{m}$$

**Sol 19: (D)** For full scale deflection

$$100 \times i_g = (i - i_g)S$$

Where 'S' is the required resistance

$$S = \frac{100 \times 1 \times 10^{-3}}{(10 - 10^{-3})}$$

$$S \approx 0.01 \Omega$$

## JEE Advanced/Boards

### Exercise 1

**Sol 1:** Let voltage at A be  $V_A$

Let current from A to B be  $i_{AB}$ . Similarly define  $i_{AC}$  by the symmetry of circuit,  $i_{AB} = i_{AC}$

$$V_B = V_A - i_{AB} (R_{AB})$$

$$= V_A - i_{AB}(1)$$

$$= V_A - i_{AB}$$

$$\text{Similarly } V_C = V_A - i_{AC}$$


$$\therefore i_{AC} = i_{AB}$$

$$\Rightarrow V_B = V_C$$

$$\Rightarrow i_{BC} = 0$$

$\Rightarrow$  We can ignore  $R_{BC}$ .

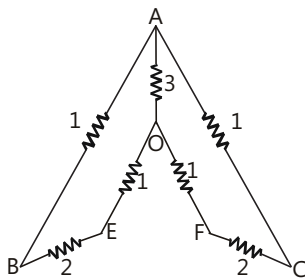Similarly we can ignore  $R_{ef}$ . Resultant circuit.




$$\Rightarrow \frac{1}{R_{\text{eff}}} = \frac{1}{2} + \frac{1}{1+2+1} + \frac{1}{1+2+1}$$

$$\frac{1}{R_{\text{eff}}} = 1$$

$\Rightarrow$  Equivalent resistance between AD =  $1\Omega$

**Sol 2:**

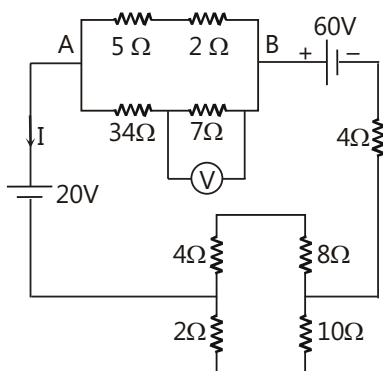

Let effective resistance across A, B be  $R_{AB}$

$$\Rightarrow \frac{1}{R_{AB}} = \frac{1}{5+2} + \frac{1}{34+7}$$

$$\Rightarrow R_{AB} = 6\Omega$$

$$\text{Similarly } \frac{1}{R_{CD}} = \frac{1}{4+8} + \frac{1}{2+10}$$

$$\Rightarrow R_{CD} = 6\Omega$$

Let current be  $I$

Writing RVL (Kirchhoff Voltage law) equation

$$60 = 20 + IR_{AB} + IR_{CD} + I(4)$$

$$40 = I(6 + 6 + 4)$$


$$\Rightarrow I = 2.5\text{ A}$$

$$V_{BA} = IR_{AD} = 2.5(6) = 15\text{ V}$$

$$\text{Voltage across } 7\Omega = \frac{7 \times V_{BA}}{7+34}$$

$$= \frac{15 \times 7}{42} = 2.5\text{ V}$$

**Sol 3:**

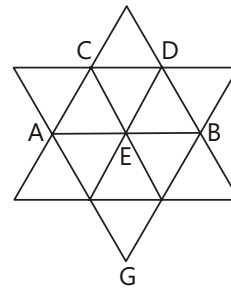

By symmetry,  $i_{CE} = i_{ED}$

$\Rightarrow$  Point E can be detached to your CED branch.

Let resistance across CD be  $R_{CD}$

$$\Rightarrow \frac{1}{R_{CD}} = \frac{1}{2} + \frac{1}{2} + \frac{1}{1} \Rightarrow R_{CD} = \frac{1}{2}\Omega$$

$$\frac{1}{R_{AC}} = \frac{1}{1} + \frac{1}{2}$$

$$R_{AC} = \frac{2}{3}\Omega$$

$$R_{DB} = \frac{2}{3}\Omega$$

$$\Rightarrow R_{ACDB} = R_{AC} + R_{CD} + R_{DB}$$

$$= \frac{1}{2} + \frac{2}{3} + \frac{2}{3}$$

$$R_{ACDB} = \frac{11}{6}\Omega$$

By symmetry,  $R_{AGB} = R_{ACDB} = \frac{11}{6} \Omega$

$$R_{AEB} = 1 + 1 = 2 \Omega$$

Let effective resistance be  $R_{\text{eff}}$ .

$$\begin{aligned} \frac{1}{R_{\text{eff}}} &= \frac{1}{R_{ACDB}} + \frac{1}{R_{AEB}} + \frac{1}{R_{AGB}} \\ &= \frac{6}{11} + \frac{6}{11} + \frac{1}{2} \\ &= \frac{35}{22} \Rightarrow R_{\text{eff}} = \frac{22}{35} \Omega \end{aligned}$$

**Sol 4:** Let current through  $11 \Omega$  be  $i_1$

$$i_1 = \frac{25+30}{11} = 5 \text{ A}$$

$$\text{Similarly } i_2 = \frac{25-20}{5} = 1 \text{ A}$$

$$i_3 = \frac{25+5}{10} = 3 \text{ A}$$

$$i_4 = \frac{25-10}{5} = 3 \text{ A}$$

$$i = i_1 + i_2 + i_3 + i_4 = 5 + 1 + 3 + 3 = 12 \text{ A}$$

Power supplied =  $V \times i$

$$= -20 \times i_2 = -20 \times 1 = -20 \text{ W}$$

Note: here  $V$  is taken  $-20\text{V}$  as it opposes the direction of current.

**Sol 5:** Let internal resistance of battery be  $R$

Current flow when  $R_1$  is connected

$$i_1 = \frac{V}{R_1 + R}$$

Power consumed

$$P_1 = i_1^2 R_1 = \frac{V^2 R_1}{(R + R_1)^2}$$

$$\text{Similarly } P_2 = \frac{V^2 R_2}{(R + R_2)^2}$$

Given  $P_1 = P_2$

$$\Rightarrow \frac{V^2 R_1}{(R_1 + R)^2} = \frac{V^2 R_2}{(R + R_2)^2}$$

$$\Rightarrow R_1 R_2^2 + 2R_1 R_2 R + R_1 R^2$$

$$= R_1^2 R_2 + 2R_1 R_2 R + R_2 R^2$$

$$\Rightarrow R^2 (R_1 - R_2) = R_1 R_2 (R_1 - R_2)$$

$$\Rightarrow R = \sqrt{R_1 R_2}$$

**Sol 6:** Path ADCB is similar to path AFEB

$$\Rightarrow i_{AD} = i_{ET}$$

Where  $i_{AD}$  is current through  $R_{AD}$ .

$$\Rightarrow V_D = V_F$$

$$\Rightarrow V_{FD} = D$$

$\Rightarrow$  Resistor  $FD$  can be removed

Similar  $EC$  can be removed

$$R_{ADCB} = 3r$$


$$R_{DFEB} = 3r$$

$$R_{AB} = r$$

Let effective resistance be  $R_{\text{eff}}$ .

$$\begin{aligned} \Rightarrow \frac{1}{R_{\text{eff}}} &= \frac{1}{R_{ADCB}} + \frac{1}{R_{AB}} + \frac{1}{R_{AFEB}} \\ &= \frac{1}{3r} + \frac{1}{r} + \frac{1}{3r} \\ \Rightarrow R_{\text{eff}} &= \frac{3r}{5} \Omega \end{aligned}$$

**Sol 7:**

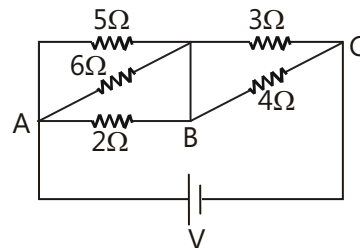

$$\frac{1}{R_{AB}} = \frac{1}{2} + \frac{1}{6} + \frac{1}{5}$$

$$R_{AB} = \frac{15}{13} \Omega$$

$$R_{BC} = \frac{20}{9} \Omega$$

Let current through circuit be  $i$

$$\Rightarrow V_{AB} = i R_{AB} = \frac{15i}{13}$$

$$V_{BC} = \frac{20i}{13}$$

Power in  $4\Omega$  is more than  $5\Omega$  across it as

$$4\Omega < 5\Omega \left( \frac{V^2}{r_1} > \frac{V^2}{r_2} \text{ if } r_1 < r_2 \right)$$

Similarly  $P_{2\Omega}$  is greater than  $6\Omega$ ,  $5\Omega$  across it

$$P_{2\Omega} = \frac{(V_{AB})^2}{2\Omega} = \left( \frac{15i}{13} \right)^2 \cdot \frac{1}{2}$$


$$P_{2\Omega} = \frac{225 i^2}{338} \Omega$$

$$P_{4\Omega} = \frac{(V_{BC})^2}{4\Omega} = \left( \frac{20i}{9} \right)^2 \frac{1}{4} = \frac{100 i^2}{81}$$

$$\frac{100}{81} > \frac{225}{338}$$

$\Rightarrow 4\Omega$  produces maximum power.

**Sol 8:**

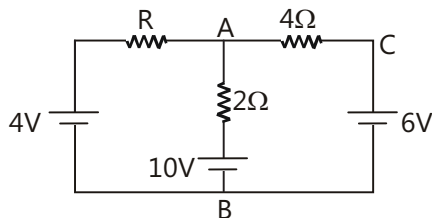

$$i_{4\Omega} = 0$$

$$\text{Given, } \Rightarrow V_{AB} = 6V$$

$$\text{But } V_{AB} = V_R + 4V$$

$$\Rightarrow V_R = 2V \quad (V_R = \text{Voltage across } R)$$

$$i_{AB} = \frac{10V - 6V}{2} = 2A$$

$$i_{AB} = i_R = 2A \quad (\because i_{4\Omega} = 0)$$

$$\Rightarrow R = \frac{V_R}{i_R} = \frac{2V}{2A} = 1\Omega$$

**Sol 9:** When both switches open,

$$i = \frac{1.5}{300 + 100 + 50} A$$

$$i = \frac{1}{3} \times 10^{-2} A$$

When both switches closed,

Voltage across  $R$ ,

$$V_R = 1000 \times i = \frac{1}{3} V$$

Current in  $200 \Omega$  ( $i_0$ )

$$= \frac{1.5 - V_R}{300} = \frac{1.5 - \frac{1}{3}}{300} = \frac{7}{18} \times 10^{-2} A$$

Current through  $R$   $i_R = i_0 - i$

$$= \frac{7}{18} \times 10^{-2} - \frac{1}{3} \times 10^{-2} = \frac{1}{18} \times 10^{-2} A$$

$$R = \frac{V_R}{i_R} = \frac{\frac{1}{3}}{\frac{1}{18} \times 10^{-2}} = 600 \Omega$$


**Sol 10:** Since resistance of voltage is  $400 \Omega$ , resistance viewed by voltmeter  $R_0$

$$\frac{1}{R_0} = \frac{1}{R} + \frac{1}{R_V}$$

$$R_V = 400 \Omega, R = 400 \Omega$$

$$\Rightarrow R_0 = 200 \Omega$$

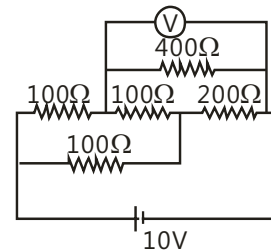Now we see there is a wheat stone bridge formed.



Hence the middle  $100 \Omega$  can be ignored

$$\Rightarrow V_{200\Omega} = \frac{200}{200 + 100} \times 10 = \frac{20}{3} V$$

$$\therefore \text{Voltmeter resonances } \frac{20}{3} V$$

**Sol 11:** Resistance of circuit

$$R = 2 \left( \frac{1}{\frac{1}{1} + \frac{1}{2}} \right) = \frac{4}{3} \Omega$$

$$\text{Current } i = \frac{V}{R} = \frac{30}{\frac{4}{3}} = \frac{45}{2} A$$

$$\text{Voltage across } 2\Omega = \frac{V}{2} = \frac{30}{2} = 15 V$$

$$i_{2\Omega} = \frac{V}{r} = \frac{15}{2} A$$

$$i_{1\Omega} = i - i_{2\Omega} = \frac{45}{2} - \frac{15}{2} = 15 A$$

$$\begin{aligned} \text{Current through AB} &= i_{1R} - i_{2R} \\ &= 15 - \frac{15}{2} = 7.5 \text{ A} \end{aligned}$$

**Sol 12:** Since current is minimum, resistance should be maximum.

⇒ All switches should be open to present short circuit.

$$R_{AB} = \frac{1}{\frac{1}{1+1}} = \frac{1}{2} \Omega$$

Resistance across switch  $S_2$ :

$$R_1 = \frac{1}{\frac{1}{9} + \frac{1}{6+3}} = \frac{9}{2} \Omega$$


Resistance of circuit

$$R = 1 + 6 + R_1 + R_{AB} = 7 + \frac{1}{2} + \frac{9}{2} = 12 \Omega$$

$$\text{Current in circuit } i = \frac{V}{R} = \frac{24}{12} = 2 \text{ A}$$

$$V_{AB} = i \cdot R_{AB} = 2 \left( \frac{1}{2} \right) = 1 \text{ V}$$

**Sol 13:**

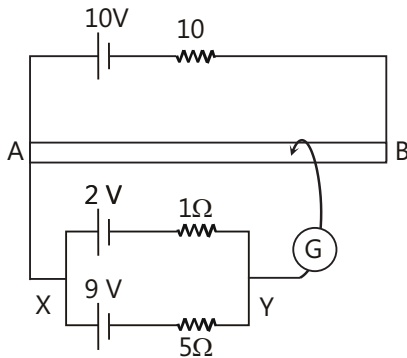

$$i_G = 0$$

$$\Rightarrow i_{AX} = 0$$

Note: here we should see XY as a system since current leaving is zero.

⇒ Current entering is zero

$$V_{AB} = V_{xy}$$

Current in XY system

$$i_{xy} = \frac{4-2}{5+1} = \frac{1}{3} \text{ A}$$

$$V_{xy} = 2 + 1 \left( \frac{1}{3} \right) = \frac{7}{3} \text{ V}$$

$$\Rightarrow V_{AP} = \frac{7}{3} \text{ V}$$

$$R_{AB} = 10 \frac{R}{m} \times 1\text{m} = 10 \Omega$$

Let  $A_p = xm$

$$R_{AP} = 10x\Omega$$

$$V_{AP} = \frac{10x}{R_{AB} + 10\Omega} \times V = \frac{10x}{10+10} \times 10$$

$$V_{AP} = 5x$$

$$\text{But } V_{AP} = \frac{7}{3} \text{ V}$$

$$\Rightarrow 5x = \frac{7}{3} \Rightarrow x = \frac{7}{15} \text{ m} = 46.67 \text{ cm}$$

**Sol 14:** Potential drop across the 40 cm wire


$$= \frac{40}{100} \times 10 \text{ v} = 4 \text{ v}$$

$$\text{Now, } 5 - ir = ir = 4$$

$$\Rightarrow 5 - i = ir = 4$$

$$\Rightarrow i = 1 \text{ A} \quad \& \quad R = 4 \Omega$$

**Sol 15:**

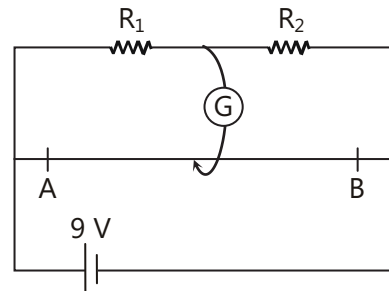

$$\frac{R_1}{R_2} = \frac{40}{60} \Rightarrow 3R_1 = 2R_2 \quad \dots (i)$$

$$\frac{R_1}{\frac{1}{\frac{1}{R_2} + \frac{1}{10}}} = 1$$

$$R_1 = \frac{R_2(10)}{10 + R_2}$$


$$R_1 R_2 = 10(R_2 - R_1) \quad \dots (ii)$$

From (i) and (ii)

$$R_1 = \frac{10}{3} \Omega; \quad R_2 = 5 \Omega$$



**Sol 16:**

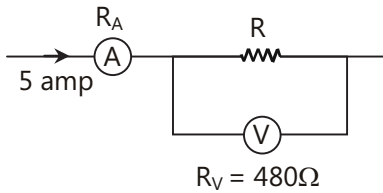


$I = 5$  ampere,  $V = 96$  V

Voltage diff. at  $R = 5 \left( \frac{480}{R + 480} \right) R = 96$

$25R = R + 480$

$R = 20 \Omega$


**Sol 17:**

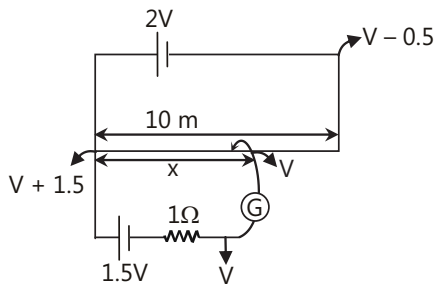

Hence  $x_i = 1.5$

$(v - x)i = 0.5$

$X = 7.5$  m

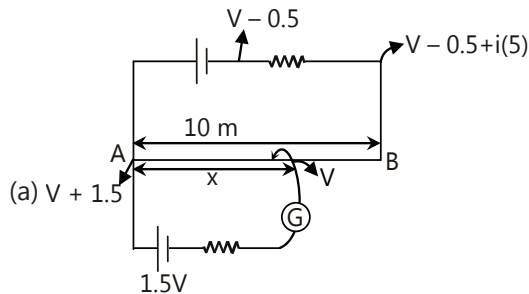

$1.5 = i \left( \frac{x}{10} \right) (30)$  ... (i)

$0.5 - i(5) = i \left( \frac{10 - x}{10} \right) 30$

$5 - 50i = i(350 - 30x)$

$5 = i(350 - 30x)$

From (i) and (ii)


$5 = 350i - 15x$

$i = \frac{2}{35}$

Putting in (i)

$1.5 = \frac{2}{35} (x) (30); \quad x = 8.75$  m


(b)

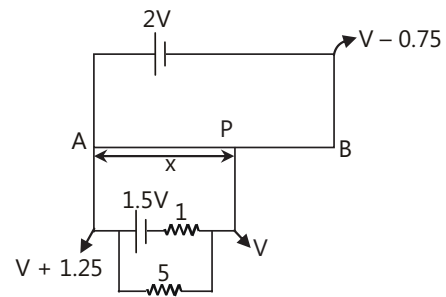

$x(3)i = 1.25$

$(10 - x) 3i = 0.75; \quad x = 6.125$  m

**Sol 18:** (a)

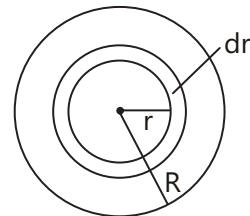

Consider a small circular strip of width  $dr$ .

Area of strip  $dA = 2\pi r dr$

Current through strip  $di = J_0 \cdot dA$

$= J_0 \left( 1 - \frac{r}{R} \right) 2\pi r \cdot dr$

$i = \int di = \int_0^R J_0 \left( 1 - \frac{r}{R} \right) 2\pi r dr$

$= 2\pi J_0 \int_0^R \left( r - \frac{r^2}{R} \right) \cdot dr = 2\pi J_0 \left( \frac{r^2}{2} - \frac{r^3}{3R} \right) \Big|_0^R$

$= 2\pi J_0 \left( \frac{R^2}{2} - \frac{R^3}{3R} \right) = \frac{\pi J_0 R^2}{3}$

... (i)

$i = \frac{AJ_0}{3} \quad (\pi R^2 = A)$

(b) Here  $J = J_0 \frac{r}{R}$


$\Rightarrow i = \int di = \int_0^R J_0 \frac{r}{R} 2\pi r dr = \frac{2\pi J_0}{3 R} r^3 \Big|_0^R = \frac{2}{3} \pi J_0 R^2$

... (ii)

$i = \frac{2AJ_0}{3}$

**Sol 19:** Initial resistance  $R_1 = 5R$

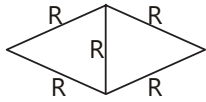Suppose two new similar resistance are added, we get a wheat stone bridge



$$\text{Resistance of bridge } R_{\text{eff}} = \frac{1}{\frac{1}{2R} + \frac{1}{2R}} = R$$

$$\therefore \text{Total resistance } R_2 = 3R$$

$$\text{Change in resistance} = 5R - 3R = 2R$$

$$R_1 : R_2 = 5 : 3$$

**Sol 20:** Let resistance be  $r$

$$(i) \Rightarrow V = V_0 - ir$$

$$\Rightarrow i = 0.2 (V_0 - ir)^{5/2}$$

$$\text{Given } i = 0.44$$

$$\Rightarrow 0.44 = (6 - 0.44r)^{5/2} \times 0.2$$

$$\left(\frac{0.44}{0.2}\right)^2 = 6 - 0.44r$$

$$r = \frac{6 - \left(\frac{0.44}{0.2}\right)^2}{0.44} = \frac{6 - 1.37}{0.44} = 10.52 \Omega$$

$$(ii) I = 0.2 \sqrt{V^2}$$

$$\Rightarrow V = \left(\frac{I}{0.2}\right)^2$$

Power dissipated in rod  $P_1 = VI$

$$P_1 = \frac{I^5}{(0.2)^5}$$

$$\text{Total power dissipated } P = \frac{3}{2} P_1$$

Power supplied by battery  $P_b = V_0 I$

$$\therefore P_b = P$$

$$\Rightarrow V_0 I = \frac{3}{2} \cdot \frac{I^5}{(0.2)^5} \Rightarrow 6 = \frac{3}{2} \cdot \frac{I^5}{(0.2)^5}$$

$$\Rightarrow I = 0.2 \cdot (4)^{5/2} = 6.4 \text{ A}$$

$$P_1 = \frac{\left(0.2(4)^{5/2}\right)^5}{(0.2)^5}$$

$$P_1 = 0.2(4)^{7/2}$$

$$P_1 = \frac{P_1}{2} = 0.1(4)^{7/2}$$

$$P_r = I^2 r = (0.2)^2 \cdot (4)^5 \cdot r$$

$$\Rightarrow 6.1(4)^{7/2} = (0.2)^2 (4)^5 \cdot r$$

$$\Rightarrow r = \frac{1}{0.4} \cdot (4)^{-3/2}$$

$$r = 0.3125 \Omega$$

$$\text{Sol 21: } R_3 = \frac{V_N}{V_N - 1}$$

$$R_1 = \frac{V_{N-1} - V_N}{V_N - 1}$$

$$\frac{R_1}{R_3} = \frac{V_{N-1} - V_N}{V_N}$$

$$\frac{R_1}{R_3} = k - 1$$

$$\text{Now } R_1 = \frac{V_0 - V_1}{i} = \frac{(k-1) - V_1}{i}$$

$$\Rightarrow \frac{V_1}{R_1} = \frac{i}{(k-1)}$$

$$R_2 = \frac{V_1}{i_1} \Rightarrow i_1 = \frac{V_1}{R_2}$$

$$R_1 = \frac{V_1 - V_2}{i - i_1} = \frac{\left(\frac{k-1}{k}\right)V_1}{i - i_1}$$

$$i - \frac{V}{R_2} = \frac{\left(\frac{k-1}{R}\right)V_1}{R_1}$$

$$i - \frac{V}{R_2} = \left(\frac{k-1}{k}\right) \frac{i}{R-1_1}$$

$$\frac{V}{R_2} = i \left(\frac{k-1}{k}\right)$$

$$\Rightarrow R_2 = \frac{VR}{i(k-1)}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{(k-1)^2}{k}$$

$$\frac{R_2}{R_3} = \frac{R_2}{R_1} \times \frac{R_1}{R_3} = \frac{k}{(k-1)}$$

**Sol 22:** Power dissipated  $P_d = 40$  watt

$$\text{Power generate } P_g = n \cdot \frac{dm}{dt} \times g \times h$$

$h =$  efficiency

$$= 0.9 \times \frac{dm}{dt} \times 10 \times 10 = 90 \frac{dm}{dt}$$

$$\text{But } P_g = P_d$$

$$\Rightarrow 40 = 90 \frac{dm}{dt}$$

$$\Rightarrow \frac{dm}{dt} = \frac{4}{9} \text{ kg/s}$$

Mass of water  $= V \times d$

$$= 200 \times 1 \text{ (1 litre = 1 kg)} = 200 \text{ kg}$$

$$\frac{200}{T} = \frac{4}{9}$$

$$T = 450 \text{ s} = 7.5 \text{ minute}$$

**Sol 23:** (i)  $V_a = \frac{3}{3+6} \times 36 = 12 \text{ V}$

$$V_b = \frac{6}{3+6} \times 36 = 24 \text{ V}$$

(ii)  $V_a = \frac{V}{2} = \frac{36}{2} = 18 \text{ V}$

$$i_{6\Omega} = \frac{18}{6} = 3 \text{ A}$$

$$i_{3\Omega} = \frac{18}{3} = 6 \text{ A}$$

$$i_{ab} = i_{3\Omega} - i_{6\Omega} = 6 - 3 = 3 \text{ A}$$

**Sol 24 :** (a)  $dr = \frac{\rho dl}{A}$ ;  $dr = \frac{\rho_0 e^{-\frac{x}{L}}}{A} \cdot dx$

$$r = \int r = \int_0^L \frac{\rho_0 e^{-\frac{x}{L}}}{A} dx = \frac{\rho_0}{A} \left[ -e^{-\frac{x}{L}} \right]_0^L$$

$$r = \frac{\rho_0 L}{A} \cdot (1 - e^{-1}) = \frac{L\rho_0}{A} \left( \frac{e-1}{e} \right)$$

$$I = \frac{V}{r} = \frac{V_0}{\frac{L\rho_0}{A} \left( \frac{e-1}{e} \right)} = \frac{V_0 A e}{L\rho_0 (e-1)}$$

$$(b) r_x = \int_0^x \frac{\rho_0 e^{-\frac{x}{L}}}{A} dx$$

( $r_x =$  resistance till a distance  $x$ )

$$= \frac{\rho_0 L}{A} \left( 1 - e^{-\frac{x}{L}} \right)$$

$$\Delta V = r_x \cdot I$$

$$= \frac{\rho_0 L}{A} \left( 1 - e^{-\frac{x}{L}} \right) \cdot \frac{\rho_0 A}{L\rho_0} \frac{1}{(1 - e^{-1})}$$

$$V_0 \left( 1 - e^{-\frac{x}{L}} \right) = \frac{V_0}{(1 - e^{-1})}$$

$$\Delta V = V_0 - V_{(R)} \quad (V(x) = \text{Potential at } x)$$

$$\Rightarrow V_{(R)} = V_0 - \Delta V$$

$$= V_0 - \frac{V_0 \left( 1 - e^{-\frac{x}{L}} \right)}{1 - e^{-1}}$$

$$V_{(R)} = V_0 \left( \frac{e^{-\frac{x}{L}} - e^{-1}}{1 - e^{-1}} \right)$$

**Sol 25 :** Voltage at 6.9 m

$$V_1 = \frac{6.9}{10} \times 2 = 1.38 \text{ V}$$

But  $V_1$  is voltage of another cell

$$\Rightarrow V_{\text{cell}} = 1.38 \text{ V}$$

The null point is  $V = 1.38 \text{ V}$

$$\text{Resistance of wire } r_w = \rho \times l = 11.5 \times 10 = 115 \text{ W}$$

Resistance at a distance  $R$ ,

$$r_x = 11.5 x$$

Voltage at  $x$

$$V_x = \frac{r_x}{r_w + 5} \times V = \frac{11.5 \times x}{120} \text{ (ii)} = \frac{11.5x}{60}$$


But  $V_x = V_{\text{cell}}$

$$\Rightarrow 1.38 = \frac{11.5x}{60} \Rightarrow x = 7.2 \text{ m}$$


## Exercise 2
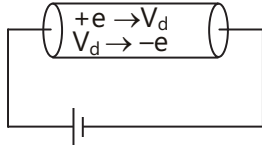
### Single Correct Choice Type

**Sol 1: (D)** We have two types of charges  $-e$  and  $+2e$



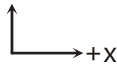When a potential different is applied both the charges drift in opposite directions.



$$\therefore i = neV_d A$$

$$i_{(+ve)} = (n)(2e) \frac{(V_d)}{4} A = \frac{neV_d A}{2}$$

$$i_{(-e)} = n(-e)(-V_d) \cdot A = n_e V_d A$$


$$i_{total} = i_{+2e} + i_{-e}$$

$$i = \frac{3}{2} neV_d A$$

Try to understand why they are getting summed up!

**Sol 2: (B)** Initially

Writing the KVL;

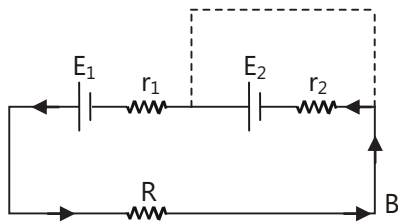

$$-E_1 + ir_1 - E_2 + ir_2 + iR = 0$$

$$\Rightarrow i = \left( \frac{E_1 + E_2}{r_1 + r_2 + R} \right) \text{ amp}$$

Now when  $E_2$  is short circuited;

$$-E_1 + i_1 r_1 + i_1 R = 0$$

$$\Rightarrow i_1 = \left( \frac{E}{r_1 + R} \right)$$


Now given that  $i_1 > i$

$$\therefore \frac{E_1}{r_1 + R} > \frac{E_1 + E_2}{r_1 + R + r_2}$$

$$E_1 r_1 + E_1 R + E_1 r_2 > E_1 r_1 + E_1 R + E_2 r_1 + E_2 R$$

$$E_1 r_2 > E_2 (R + r_1)$$

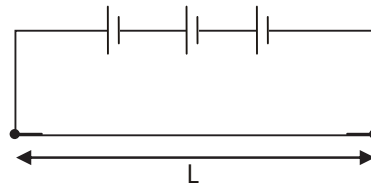**Sol 3: (B)** Power initially =  $\frac{V^2}{R} = \frac{(3)^2}{R}$



Now when length is doubled,

$$P_{final} = 2 P_{initial}$$


$$P_{final} = 2 P_{initial} \left[ R = \frac{3L}{A} \right]$$

$$\therefore \frac{V_1^2}{R_f} = 2 \cdot \frac{(3)^2}{R}$$

$$\therefore V = \sqrt{4 \times (3)^2} = 2 \times 3$$

$$N = 6$$

**Sol 4: (A)**

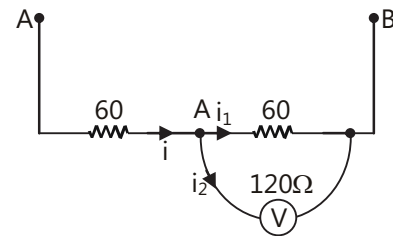

$$R_{eff} = 60 \Omega + (60 \parallel 120) = 60 \Omega + 40 \Omega$$

$$R_{eff} = 100 \Omega$$

$$i = \frac{120 \text{ Volt}}{100 \Omega} = 1.2 \text{ amp}$$

$$60 i_1 = 120 i_2$$

$$i_1 = 2i_2$$

.....(i)


and also at junction A;  $i = i_1 + i_2$

$$i = 2i_2 + i_2$$


$$i_2 = \frac{i}{3} = 0.4 \text{ amp}$$

$$\therefore V \text{ across voltmeter} = (0.4) (120) = 48 \text{ V}$$

**Sol 5: (B)** Now we can remove resistor OO' because of symmetry property.

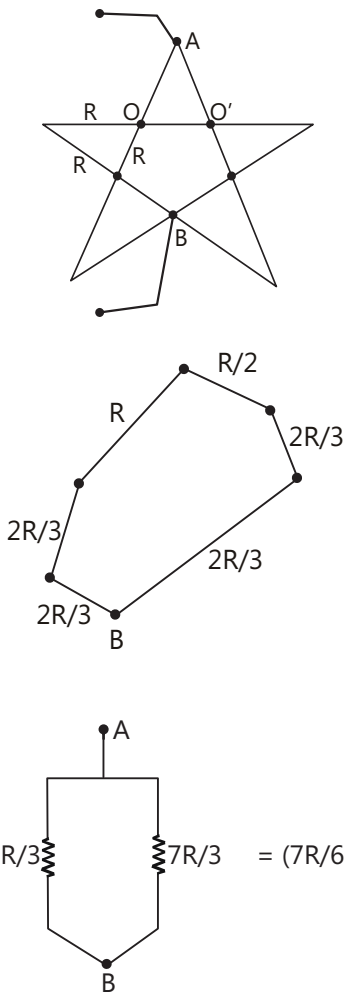

**Sol 6: (B)** In Mesh A, Applying KVL;

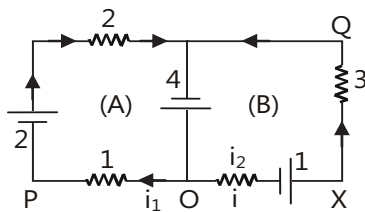

$$i_1 - 4 + 2i_1 - 2 = 0$$

$$3i_1 = 6$$

$$\Rightarrow i_1 = 2 \text{ amp}$$

Now same for mesh 2;

$$-2i_2 + 1 - 3i_2 + 4 = 0$$

$$\Rightarrow i_2 = 1 \text{ amp}$$


Now applying voltage drop along POXQ;

$$V_p + i_1(1) - 2i_2 + 1 - 3i_2 = V_Q$$

$$V_p - V_Q = 5i_2 - i_1 - 1 = 5 - 2 - 1$$

$$V_{PQ} = 2V$$

**Sol 7: (A)**

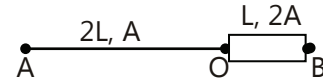

$$R_1 = \frac{\rho \cdot 2L}{A} \quad R_2 = \frac{\rho \cdot 2L}{2A}$$

$$R_1 = 2 \left( \frac{\rho L}{A} \right); \quad R_2 = \frac{1}{2} R_x \left[ \because R = \frac{\rho L}{A} \right]$$

$$R_1 = 2R$$

$$i = \frac{V_A - V_B}{R_1 + R_2} = \frac{8 - 1}{2R + \frac{R}{2}} = \frac{7}{\frac{5R}{2}} = \left( \frac{14R}{5R} \right)$$

$$V_A - iR_1 = V_0$$

$$8 - \left( \frac{14}{5R} \right) (2R) = V_0$$

$$V_0 = 8 - \frac{28}{5} = 2.4 \text{ V}$$

**Sol 8: (C)**  $\frac{P}{V} = \frac{EeVd}{V}$

$$J = neV_d \Rightarrow \frac{P}{V} = EJ$$

**Sol 9: (C)**  $IR = ir$

$$I = 10 \text{ mA}$$

$$R = 9\Omega + 0.9\Omega = 9.9\Omega$$


$$r = 0.1\Omega$$

$$\Rightarrow i = \frac{10 \times 9.9}{0.1} = 990 \text{ mA}$$

$$\text{Total current} = i + I = 990 + 10 = 1A$$

**Sol 10: (C)** For wheatstone bridge,

$$R_1 R_4 = R_2 R_3$$

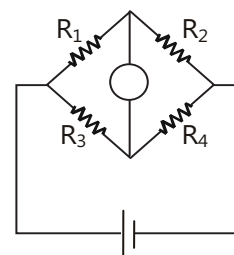

It is independent of emf

Let  $r = KR$

$$\Rightarrow r_1 r_4 = K^2(R_1 R_4) = K^2(R_2 R_3) = r_2 r_3$$

So it is still balance

Even if battery and galvanometer are interchanged, still it is balanced.

**Sol 11: (B)**  $625(P) = QS$

$$(625 + 51) = PS$$


$$\Rightarrow 625 \cdot \frac{P}{Q} = 676 \left( \frac{Q}{P} \right); \Rightarrow \frac{P}{Q} = \sqrt{\frac{676}{625}}$$

$$\frac{P}{Q} = \frac{26}{25}$$

$$S = 625 \frac{P}{Q} = 625 \times \frac{26}{25} = 650 \Omega$$

**Sol 12: (D)** Number of free electrons is constant for ohmic resistor.

**Sol 13: (A)**

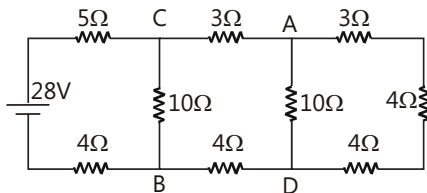

$$R_{AD} = \frac{1}{\frac{1}{10} + \frac{1}{3+4+3}} = 5\Omega$$

$$R_{CB} = \frac{1}{\frac{1}{10} + \frac{1}{3+5+2}} = 5\Omega$$

$$i = \frac{28}{5+5+4} = 2A$$

Current through  $5\Omega$  is  $2A$

$$R_{CADB} = 3+5+2 = 10\Omega$$

$$\therefore R_{CADB} = R_{CB}$$

$$\Rightarrow i_{CA} = i_{CB} = \frac{i}{2} = 1A$$

$$V_{CA} = 1 \times 3 = 3V$$

$$V_{CB} = 1 \times 10 = 10V$$

$$V_{AB} = V_{CB} - V_{CA} = 10 - 3$$

$$V_A - V_B = 7V$$

$$\text{Sol 14: (C)} \text{ If } V \text{ was ideal, } R = \frac{V_0}{i_0} = \frac{20}{4} = 5\Omega$$

$\therefore V$  is not ideal,  $i < i_0$

$$\Rightarrow R > R_0$$

$$\Rightarrow R > 5\Omega$$

**Multiple Correct Choice Type**


**Sol 15: (A, B, C, D)** Current is constant across the cross-section.

$$E \propto \frac{1}{A}; \quad r \propto \frac{1}{A}$$

$$\Rightarrow i^2 r \propto \frac{1}{A}$$

$\therefore$  Heat at  $Q >$  heat at  $P$

**Sol 16: (A, D)**

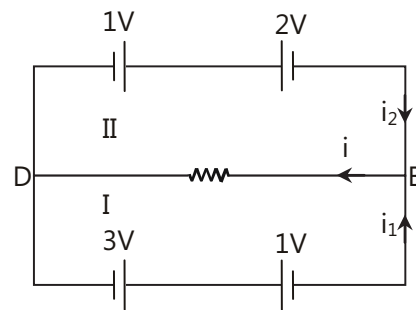

Let  $V_D = 0$

$$3V - 1V = i_1(3 + 1) + 2I \text{ (for loop I)}$$

$$1V - 2V = i_2(2 + 1) + 2I \text{ (for loop II)}$$

$$I = i_1 + i_2$$

$$\Rightarrow 2V = i_1(4) + 2(i_1 + i_2)$$

$$\Rightarrow 6i_1 + 2i_2 = 2 \quad \dots (i)$$

$$-1V = 3i_2 + 2(i_1 + i_2)$$

$$\Rightarrow 2i_1 + 5i_2 = -1 \quad \dots (ii)$$

$$\Rightarrow i_2 = \frac{-5}{13} A \text{ (from i and ii)}$$

$$i_1 = \frac{6}{13} A$$

$$V_B - V_D = 2(I) = 2(i_1 + i_2)$$

$$= 2 \left( \frac{6}{13} - \frac{5}{13} \right) = \frac{2}{13} V$$

$$\Rightarrow V_D - V_B = \frac{-2}{13} V$$

$$\Delta V_G = E_G - i_1 B_G = 3V - \frac{6}{13} (3) V = \frac{21}{13} V$$

$$\Delta V_H = E_H + i_1 R_H = 1 + \frac{6}{13} (1) = \frac{19}{13} V$$

**Sol 17 : (B, C)** Let range of voltage be V

Let resistance added be R

$$V = i(R + r)$$

For  $R \gg r$ ,

$$V = iR; i = 50 \mu A = 50 \times 10^{-6} A$$

$$\text{For } 200 \text{ k}\Omega, V = 10V$$

$$\text{For } 10 \text{ k}\Omega, V = 0.5V$$

Let range of ammeter be I

Let resistance in series be R

$$\text{Voltage } V = 50 \times 10^{-6} \times 100 = 5 \text{ mV}$$

$$\text{For } i = \frac{V}{R} \quad (R \ll r)$$

$$\text{For } R = 1 \Omega, I = 5 \text{ mA}$$

For  $R = 1 \text{ k}\Omega, R \gg r$ , so cannot be ammeter

**Sol 18 : (A, B, C)** For  $R = 120 \Omega$

Potential across potentiometers

$$\Delta V_p = \frac{75(20)}{75+5+120} = \frac{75(20)}{200} = 7.5 \text{ V}$$

For  $V < \Delta V_p$

V can be measured

**Sol 19 : (A, D)** Current is constant, hence charge crossing cross section

$$J = nev$$

J is not constant  $\Rightarrow v_d$  variable

**Sol 20: (A, D)** Ammeter should have small resistance and voltmeters large

### Assertion Reasoning Type

**Sol 21: (D)**  $JE = \frac{iR^2}{V}$  (V = volume)

$$\Rightarrow E \propto R^2$$

$\therefore$  Statement-I is false


**Sol 22: (D)** If a battery of higher emf is placed across it, e.m.f. of given battery < potential difference across it

**Sol 23: (A)** Statement-II explains statement-I

### Comprehension type

#### Paragraph 1

**Sol 24: (B)**  $E = B \frac{dA}{dt}$

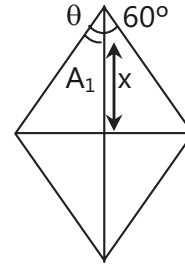

$$A = 4A_1$$

$$A = \frac{1}{2} \cdot x (x \tan \theta)$$

$$= \frac{x^2}{2} \tan \theta \left( \theta = \frac{60^\circ}{2} = 30^\circ \right)$$

$$\frac{dA_1}{dt} = x \tan \theta - \frac{dx}{dt} = xv \tan \theta$$

$$x = a \cos \theta$$

$$\Rightarrow \frac{dA_1}{dt} = av \sin \theta$$

$$\frac{dA}{dt} = 4av \sin \theta$$

$$\Rightarrow E = B \frac{dA}{dt} = 4avB \sin \theta = 4avB \sin 30^\circ = 2avB$$

**Sol 25: (B)**  $i = \frac{E}{R} = \frac{2BaV}{R}$

**Sol 26: (A)**  $i = \frac{B \frac{dA}{dt}}{R}$

$$\frac{dQ}{dt} = \frac{B}{R} \cdot \frac{dA}{dt}$$

$$\Rightarrow \Delta Q = \frac{B}{R} \Delta A = \frac{B}{R} (a^2)$$

$$\Delta Q = \frac{a^2 B}{B}$$

**Paragraph 2**

**Sol 27: (A)** Just after pressing switch,  $I_2 = 0$  as inductor doesn't pass current through it initially.

$$\therefore I_1 = I_3 = \frac{V}{R_1 + R_2} = \frac{10}{2+6} = \frac{10}{8} \text{ A}$$

**Sol 28: (A)** After long time, inductor acts as short circuit.

$$\therefore I_2 = \frac{R_3 I_1}{R_3 + R_2}$$

$$I_1 = \frac{E}{R_1 + \frac{R_2 \times R_3}{R_2 + R_3}} = \frac{10}{2 + \frac{3 \times 6}{3+6}} = 2.5 \text{ A}$$

**Sol 29: (D)**  $I_2 = \frac{6 \times 2.5}{9} \left( I_2 = \frac{R_3 I_1}{R_2 + R_3} \right)$

$$I_2 = \frac{5}{3} \text{ A}$$

**Sol 30: (C)** Even after releasing switch, inductor still tries to continue the same current

$$\Rightarrow I_2 = \frac{10}{6} \text{ A}$$

**Match the Columns**

**Sol 31:** A  $\rightarrow$  p; B  $\rightarrow$  q; C  $\rightarrow$  r; D  $\rightarrow$  p

**Previous Years' Questions**


**Sol 1: (A)**  $R_{PQ} = \frac{5}{11}r$ ,  $R_{QR} = \frac{4}{11}r$  and  $R_{PR} = \frac{3}{11}r$

$\therefore R_{PQ}$  is maximum.

**Sol 2: (C)** BC, CD and BA are known resistance.

The unknown resistance is connected between A and D.

**Sol 3: (A)**

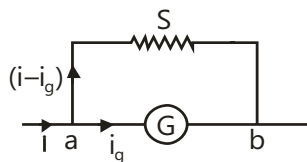

$$V_{ab} = i_g \cdot G = (i - i_g)$$

$$\therefore i = \left( 1 + \frac{G}{S} \right) i_g$$

Substituting the values, we get,  $i = 100.1 \text{ mA}$

**Sol 4: (C)** Current in the respective loop will remain confined in the loop itself.

Therefore, current through  $2\Omega$  resistance = 0

**Sol 5: (A)** Current flowing through the bars is equal. Now, the heat produced is given by

$$H = I^2 R t \text{ or } H \propto R$$

$$\text{or } \frac{H_{AB}}{H_{BC}} = \frac{R_{AB}}{R_{BC}} = \frac{(1 \sqrt{2}r)^2}{(1 \sqrt{r})^2} \text{ (as } R \propto \frac{1}{A} \propto \frac{1}{r^2} \text{)}$$

$$= \frac{1}{4} \text{ or } H_{BC} = 4H_{AB}$$

**Sol 6: (B)**  $\tau = CR$


$$\tau = (C_1 + C_2)(R_1 + R_2) = 18 \mu\text{s}$$

$$\tau_2 = \left( \frac{C_1 C_2}{C_1 + C_2} \right) \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \frac{8}{6} \times \frac{2}{3} = \frac{8}{9} \mu\text{s}$$

$$\tau_3 = (C_1 + C_2) \left( \frac{R_1 R_2}{R_1 + R_2} \right) = (6) \left( \frac{2}{3} \right) = 4 \mu\text{s}$$


**Sol 7: (C)** From Y to X charge flows to plates a and b.
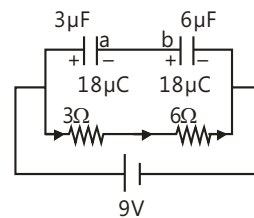
$$(q_a + q_b)_i = 0, (q_a + q_b)_f = 27 \mu\text{C}$$



Initial Figure

(When switch was open)

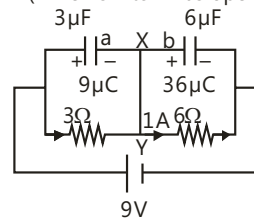

Final Figure

(When switch is closed)

$\therefore 27 \mu\text{C}$  charge flows from Y to X.

**Sol 8: (C)** Applying  $P = \frac{V^2}{R}$ ,  $R_1 = 1 \Omega$ ,  $R_2 = 0.5 \Omega$

and  $R_3 = 2 \Omega$

$$V_1 = V_2 = V_3 = 3V$$

$$\therefore P_1 = \frac{(3)^2}{1} = 9 \text{ W}$$



$$P_2 = \frac{(3)^2}{0.5} = 18 \text{ W and } P_3 = \frac{(3)^2}{2} = 4.5 \text{ W}$$

$$\therefore P_2 > P_1 > P_3$$

**Sol 9: (C)**  $R = \frac{\rho(L)}{A} = \frac{\rho L}{tL} = \frac{\rho}{t}$

i.e. R is independent of L.

**Sol 10: (D)** With increase in temperature, the value of unknown resistance will increase.

In balanced Wheat stone bridge condition,  $\frac{R}{X} = \frac{l_1}{l_2}$


Hence R = Value of standard resistance

X = value of unknown resistance

To take null point at same point or  $\frac{l_1}{l_2}$  to remain unchanged  $\frac{R}{X}$  should also remain unchanged.

Therefore, if X is increasing R, should also increase.

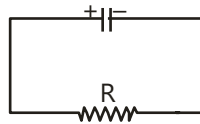**Sol 11: (B, D)** The discharging current in the circuit is,  $i = i_0 e^{-\tau/CR}$



Hence,  $i_0 = \text{initial current} = \frac{V}{R}$

Here, V is the potential with which capacitor was charged.

Since, V and R for both the capacitors are same, initial discharging current will be same, but non-zero.

Further,  $\tau_c = CR$

$C_1 < C_2$  or  $\tau_{C_1} < \tau_{C_2}$

or  $C_1$  loses its 50% of initial charge sooner than  $C_2$ .

**Sol 12: (B, C)** To increase the range of ammeter a parallel resistance (called shunt) is required which is given by

$$S = \left( \frac{i_x}{i - i_g} \right) G$$

For option (C)

$$S = \left( \frac{50 \times 10^{-6}}{5 \times 10^{-3} - 50 \times 10^{-6}} \right) (100) = 1 \Omega$$

To change it in voltmeter, a high resistance R is put in series where R is given by  $R = \frac{V}{i_g} - G$

For option (B)  $R = \frac{10}{50 \times 10^{-6}} - 100 \approx 200 \text{ k}\Omega$

**Sol 13: (A, B, D)** At 0 K, a semiconductor becomes a perfect insulator. Therefore, at 0 K, if some potential difference is applied across an insulator or semiconductor, current is zero. But a conductor will become a super conductor at 0 K. Therefore, current will be infinite. In reverse biasing at 300 K through a p-n junction diode, a small finite current flows due to minority charge carriers.

**Sol 14: (A, D)**  $R_{\text{total}} = 2 + \frac{6 \times 1.5}{6 + 1.5} = 3.2 \text{ k}\Omega$

(a)  $I = \frac{24 \text{ V}}{3.2 \text{ k}\Omega} = 7.5 \text{ mA} = I_{R_1}$

$$I_{R_2} = \left( \frac{R_L}{R_L + R_2} \right) I$$

$$I = \frac{1.5}{7.5} \times 7.5 = 1.5 \text{ mA}$$

$$I_{R_L} = 6 \text{ mA}$$

(b)  $V_{R_L} = (I_{R_L})(R_L) = 9 \text{ V}$

(c)  $\frac{P_{R_1}}{P_{R_2}} = \frac{I_{R_1}^2 R_1}{I_{R_2}^2 R_2} = \frac{(7.5)^2 (2)}{(1.5)^2 (6)} = \frac{25}{3}$

(d) When  $R_1$  and  $R_2$  are inter changed then

$$\frac{R_2 R_L}{R_2 + R_L} = \frac{2 \times 1.5}{3.5} = \frac{6}{7} \text{ k}\Omega$$

Now potential difference across  $R_L$  will be


$$V_L = 24 \left[ \frac{6/7}{6 + 6/7} \right] = 3 \text{ V}$$

Earlier it was 9V


Since,  $P = \frac{V^2}{R}$  or  $P \propto V^2$

In new situation potential difference has been decreased three times. Therefore, power dissipated will decrease by a factor of 9.

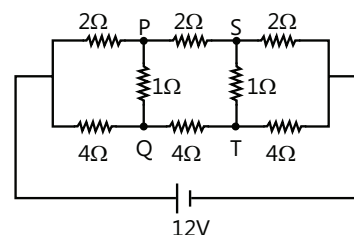**Sol 15: (A, B, C, D)** The circuit can be simplified as



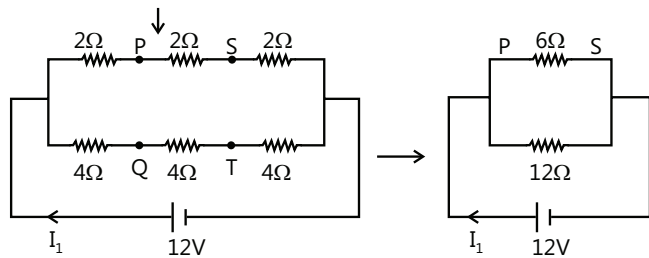Because of symmetry no current through  $1\Omega$



$$R_{eq} = \frac{12 \times 6}{12 + 6} = 4\Omega$$

$$I_1 = \frac{12}{4} = 3A \quad ; \quad I_2 = \frac{2}{3} \times 3 = 2A$$

Here we have

$$V_S - V_Q = -4 \quad \text{i.e.,} \quad V_S < V_Q$$

**Sol 16: (A, B, D)**  $V_1 = \frac{R_1(V_1 + V_2)}{R_1 + R_3} \Rightarrow V_1 R_3 = V_2 R_1$

$$V_2 = \frac{R_3(V_1 + V_2)}{R_1 + R_3} \Rightarrow V_2 R_1 = V_2 R_3$$

**Sol 17: (C)**  $R = \frac{x}{100 - x} 90$

$$\therefore R = 60\Omega$$

$$\frac{dR}{R} = \frac{100}{(x)(100 - x)} dx$$

$$\therefore dR = \frac{100}{(40)(60)} 0.1 \times 60 = 0.25\Omega$$

**Sol 18: (C)** For infinite the,

$$E = \frac{\lambda}{2\pi\epsilon r}$$

$$\Rightarrow dV = \frac{-\lambda}{2\pi\epsilon r} dr$$

Current through an elemental shell ;


$$I = \frac{|dV|}{dR} = \frac{\frac{\lambda}{2\pi\epsilon r} dr}{\frac{1}{\sigma} \times \frac{dr}{2\pi r \ell}} = \frac{\lambda \sigma \ell}{\epsilon}$$

This current is radially outwards so ;

$$\frac{d}{dt}(\lambda \ell) = \frac{-\lambda \sigma \ell}{\epsilon} \Rightarrow \frac{d\lambda}{\lambda} = -\left(\frac{\sigma}{\epsilon}\right) dt$$

$$\Rightarrow \lambda = \lambda_0 e^{-(\sigma/\epsilon)t}$$

$$\text{So, } j = \frac{I}{2\pi r \ell} = \frac{\lambda \sigma}{2\pi \epsilon r} = \left(\frac{\lambda_0 \sigma}{2\pi \epsilon r}\right) e^{-(\sigma/\epsilon)t}$$

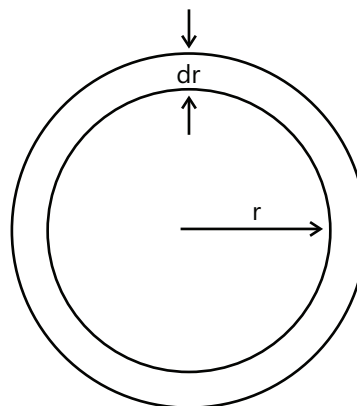

**Sol 19: (A, C)** For maximum voltage range across a galvanometer, all the elements must be connected in series.


For maximum current range through a galvanometer, all the elements should be connected in parallel.

**Sol 20: (A, B, C, D)** At  $t = 0$  voltage across each capacitor is zero, so reading of voltmeter is -5 Volt.

At  $t = \infty$ , capacitors are fully charged. So for ideal voltmeter, reading is 5 Volt.

At transient state.
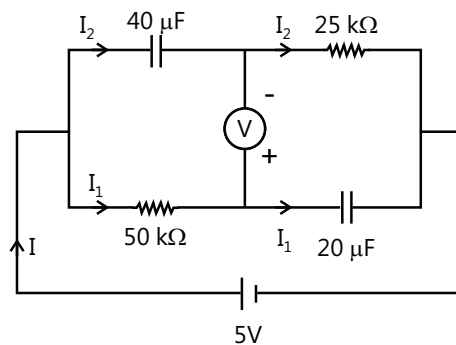
$$I_1 = \frac{5}{50} e^{-\frac{t}{\tau}} \text{ mA}, \quad I_2 = \frac{5}{25} e^{-\frac{t}{\tau}} \quad \text{and} \quad I = I_1 + I_2$$



Where  $\tau = 1$  sec

So  $I$  becomes  $1/e$  times of the initial current after 1 sec.

The reading of voltmeter at any instant

$$\Delta V_{40\mu F} - \Delta V_{50k\Omega} = 5 \left(1 - e^{-\frac{t}{\tau}}\right) - 5e^{-\frac{t}{\tau}}$$

So at  $t = \log 2$  sec, reading of voltmeter is zero.